

Introduction to Verilog HDL

Behavioral description of logic circuits
with Verilog HDL (IEEE1364)

1. Overview

Steps of Learning HDL

- Goal of this class
 - Understanding a description for logic synthesis
 - Understanding a description for simulation
- Goal of Integrated Circuit Design and Practice
 - Understanding an architecture of microprocessors with HDL including
 - BUS
 - Memory
 - Instruction set
 - Various arithmetic algorithm
 - Parallel processing and pipeline control
- Moreover...
 - Usage of intellectual properties (IPs)

References in Japanese

- 深山正幸他 「HDLによるVLSI設計」第2版, 共立出版 ISBN 4-320-12027-2
- You can find many references on web sites, for example,
 - <http://cas.eeddept.kobe-u.ac.jp/~arai/Verilog/chap5.html>
 - <https://furien.jp/columns/303/>


HDL Simulator

- ModelSim - Intel FPGA Edition (Lite)



<https://www.intel.co.jp/content/www/jp/ja/software/programmable/quartus-prime/model-sim.html>

- See Appendix 1a and 1b.

LSI/FPGA design flow with HDL

 

The purpose of HDL description

  


Logic tester in Kanazawa University: <http://jaco.ec.t.kanazawa-u.ac.jp/edu/vlsi/ni6570/>

2. HDL description in RTL

RTL: register transfer level

means the level of detail which describes the digital processing and controlling the signal flow for each clock edge. The logic circuit can be absolutely synthesized from the description.

 Combinational logic with assign statement



16bit Adder

```

module adder16 (a, b, sum, co);
    // 16 bit Adder
    input  [15:0] a, b;
    output [15:0] sum;
    output          co;

    wire  [15:0] a, b, sum;
    wire          co;

    assign {co, sum} = a + b;
endmodule
    
```


module adder16 (a, b, sum, co); ← Module declaration
 // 16 bit Adder ← // Comment
 input [15:0] a, b; } ← Port declaration
 output [15:0] sum; } (input | output) [MSB:LSB]
 output co; } ← Note: [MSB:LSB] is optional for 1bit port

wire [15:0] a, b, sum; } ← Type declaration
 wire co; } ← Note: You can omit the type declaration of wire.

assign {co, sum} = a + b; ← An assign statement for logic value of wire
 Note: The assignment statements are concurrently
 executed when the value of the right side is updated.
 {high-order bits, low-order bits} is a concatenation
 operator.

No ";" after endmodule The end of statement

 Combinational logic with always statement



16bit Adder

```

module adder16 (a, b, sum, co);
  input  [15:0] a, b;
  output [15:0] sum;
  output          co;

  wire  [15:0] a, b;
  reg   [15:0] sum;
  reg           co;

  always @(a, b) begin
    {co, sum} <= a + b;
  end
endmodule

```

Module declaration

Port declaration

Type declaration of reg (register) and wire

The always-block is started when the value in **@(variables)** is updated.

The multiple always-block works simultaneously.

An procedural assignment for logic value of reg.

Note: All "<=" statements in a always-block are executed when the always statement is asserted. An "<=" statement is also called **non-blocking assignment**.

No ";" for end and endmodule

Assignment and variable types in RTL

Statement	Type restriction	Location	Execution timing
<code>assign a = b;</code>	left side: wire right side: reg or wire	outside of always block	When the right side is updated.
<code>a <= b;</code> (non-blocking assignment)	left side: reg right side: reg or wire	inside of always block	When the always block is asserted.

Note: Normally, the register (D-FF) is synthesized by the non-blocking assignment to the reg variable, however, the always block which does not synchronize the clock does not generate the register.



Conditional assign statement

Verilog HDL

```
assign x = (c == 1'b1) ? a : b;
```

C

```
if (c == 1) x = a;  
else x = b;
```

  


Note: The non-blocking assignment is normally used to describe the functions of the information processing. The assign statement is useful to output the value of the registers from the output port.

Variable types in RTL

Type declaration	Application	Remarks
<code>reg a;</code> <code>reg [15:0] a;</code>	Logic variable of the register	left side of <code><=</code>
<code>wire a;</code> <code>wire [15:0] a;</code>	Logic variable of the wire The declaration of wire can be omitted.	left side of assign <code>=</code>
<code>integer a;</code>	Do not use the integer for the logic variables. This type is dedicated to the bit number or loop counter.	Do not assign to reg and wire.

Constant and Literal

Statement	Description	Remarks
parameter a = 0;	Declaration of constant	A type of parameter depends on the initial number.
a <= 8'b00001111;	Binary number	
a <= 8'd15;	Decimal number	
a <= 8'h0f;	Hexadecimal number	

 

Sequential logic with always statement

16bit Accumulator


```

module integrator16 (a, clk, x);
  input      clk;
  input [15:0] a;
  output [15:0] x;

  wire      clk;
  wire [15:0] a;
  reg [15:0] ar, x;

  always @(posedge clk) begin
    ar <= a;
    x <= ar + x;
  end
endmodule

```

 

The always-block is started in synchronization with the edge of the clk signal. The rise edge and fall edge is specified by using the keyword "posedge" or "negedge".

An assign statement for logic value of reg. A register circuit is synthesized by the edge sensitive non-blocking assignment.

Note: All "<=" statements in a always-block are executed when the always statement is asserted.

The multiple "<=" is simultaneously executed. Thus, the value of the register "ar" in 2nd line is different from the 1st one. This is really different from the programming language See next slide.


Non-blocking assignment in always block

Synchronized assignment

```
always @(posedge clk) begin
  b <= a + b;
  c <= b - c;
end
```

after clock edge


 
before clock edge
(This value is calculated by last edge.)



The result is different from a procedural language.

If $a = 1$, $b = 1$, and $c = 1$ before the clock edge, b and c on the left is updated $b = 2$ and $c = 0$ after the clock edge.

Expected circuit for the description

  

Truth table with case statement

3bit Decoder

```
module dec3 (address, word);
  input  [2:0] address;
  output [7:0] word;

  wire  [2:0] address;
  reg   [7:0] word;

  always @(address) begin
    case (address)
      3'b000 : word <= 8'b00000001;
      3'b001 : word <= 8'b00000010;
      3'b010 : word <= 8'b00000100;
      3'b011 : word <= 8'b00001000;
      3'b100 : word <= 8'b00010000;
```

3'b 3bit binary number
4'h0 4bit hexadecimal number

address	word
000	00000001
001	00000010
010	00000100
011	00001000
100	00010000
101	00100000
110	01000000
111	10000000


```
      3'b101 : word <= 8'b00100000;
      3'b110 : word <= 8'b01000000;
      3'b111 : word <= 8'b10000000;
      default : word <= 8'bxxxxxxxx;
    endcase
  end
endmodule
```

A "default" assignment is recommended in a case statement.

Conditional branch with case statement

4bit MUX
 
```
module mux4 (a, b, c, d, sel, x);  
  input  [3:0] a, b, c, d;  
  input  [1:0] sel;  
  output [3:0] x;  
  
  wire  [3:0] a, b, c, d;  
  wire  [1:0] sel;  
  reg   [3:0] x;  
  
  always @(a or b or c or d or sel) begin  
    case (sel)  
      2'b00 : x <= a;  
      2'b01 : x <= b;  
      2'b10 : x <= c;  
      2'b11 : x <= d;
```



```
      default : x <= 4'bxxxx;  
    endcase  
  end  
endmodule
```

State transition with if-else statement

8bit Binary counter

```

module count8 (clk, rst, en, q, co);
  input      clk, rst, en;
  output [7:0] q;
  output      co;

```

```

  wire      clk, rst;
  wire      co;
  reg [7:0] q;

```


```

  always @(posedge clk) begin
    if (rst == 1'b0)
      q <= 8'b00000000;
    else
      q <= q + en;

```

State transition driven by the clock edge. The processing contents is written in another always-block or assign statement.

Synchronous reset

 

```

  end
  assign co = &q;
endmodule

```

Processing content:
 Unary operation "&" performs AND operation for all digit.
 Thus, if q = 255, then the "1" is outputted from co port.

Asynchronous reset


4bit Johnson counter

```


module jcnt4 (clk, rst_b, pr_b, q);
  input      clk, rst_b, pr_b;
  output [3:0] q;
  reg [3:0] q;

  always @(negedge rst_b or negedge pr_b or posedge clk) begin
    if (!rst_b) begin
      q <= 4'h0; ← Asynchronous reset
    end
    else if (!pr_b) begin
      q <= 4'hf;
    end
    else begin
      q <= q << 1;
      q[0] <= ~q[3];
    end
  end
end
endmodule

```

 

Hierarchically organized description

 

Structured description and instantiation

```

module sub(A, B, I, F);
  input  [15:0]  A, B;
  input          I;
  output [16:0]  F;

  wire  [15:0]  A, B;
  wire          I;
  reg   [16:0]  F;
  reg   [15:0]  CMP;

  add16 i0(.a(A), .b(CMP), .ci(I), .sum(F));

  always @(B, I) begin
    if(I == 1'b0)
      CMP <= B;
    else
      CMP <= ~B;
  end
endmodule

```

Call


```

module add16 (a, b, ci, sum);
  input  [15:0]  a, b;
  input          ci;
  output [16:0]  sum;

  wire  [15:0]  a, b;
  wire          ci;
  reg   [16:0]  sum;

  always @(a, b, ci) begin
    sum <= a + b + ci;
  end
endmodule

```

 

4. HDL description of test bench

The test bench includes the DUT (Device Under Test) or UUT (Unit Under Test), the sequence of the input vector, and the directive to the simulator, which can be described by HDL code in any level of detail.


HDL Simulation

- Functional simulation
 - Logic simulation without respect to a gate propagation delay and the wiring delay.
 - A functional simulation is performed to verify the HDL description.
- Timing simulation
 - The logic simulation with considering a delay times
 - A timing simulation is performed to detect the malfunction.
 - After synthesis
 - A gate propagation delay is considered and the wiring delay is approximately estimated from a statistical data.
 - After place and route
 - A gate propagation delay and the accurate delay time of each wire are considered.

Structure of Test bench

- A test bench includes input vectors, instances of DUT, and directives to specify output signals.
- A test bench is not only an external system of DUT, but also a module in an uppermost layer. Thus, the test bench does not have any port.

Test bench

 

Declaration and Instantiation

```
`timescale 1ns/1ns  
module tb_count8;  
    reg          r_clk, r_rst, r_en;  
    wire [7:0]   w_q;  
    wire         w_co;  
    integer     i;  
  
    // Half Cycle of Clock  
    parameter hf_cycle = 50;  
  
    // Instance of Module count8  
    count8 i0(.clk(r_clk), .rst(r_rst), .en(r_en), .q(w_q), .co(w_co));
```

← unit / precision, It has no effect in synthesis.

← No port in a test bench.

} The type of signals are declared to be "reg" for input of DUT, and to be "wire" for output of DUT.

← The parameter definition of half cycle is useful for the

←

Continuing

DUT(Device under Test)

Generation of test vector


```
// Test Vectors
initial begin
    r_rst <= 1'b1;
    r_en <= 1'b1;
    #(2*hf_cycle) r_rst <= 1'b0;
    #(2*hf_cycle) r_rst <= 1'b1;
    #(512*hf_cycle) r_en <= 1'b0;
end
```

Waiting time

```
// Clock Generation
initial begin
    r_clk <= 1'b0;
    for (i = 0; i < 519; i = i + 1)
        #(hf_cycle) r_clk <= ~ r_clk;
    $finish;
end
endmodule
```

The simulation is started from initial block.

Finish of Simulation.

 

"initial" block

- An "initial" statement is performed only once after starting the simulation.
 - **Important:** Do not use "initial" statement in a description to synthesize a circuit, because the real circuit cannot wait the initialization process to finish by oneself.
 - The initialization process of can be described in an always-block started by the external signal such as PoR (Power-on reset) or CS (chip select).

Blocking assignment in always-block

- A blocking assignment is sequentially executed in an instruction order.
- Do not use a blocking assignment for the synthesis, because the blocking assignment in the always-block generates a latch circuit and it is difficult to determine the ordering relations between the blocks.

assignment state	assign b = a; assign c = b;	c != a
Non-blocking assignment	always @(a, b) begin b <= a; c <= b;	c != a
Blocking assignment	always @(a, b) begin b = a; c = b;	c == a

5. Example of Lticka circuit

Learn the simple example of HDL description in RTL and test bench.

Top module

```
module LED(WIDTH, CLK, RST_B, OUT);

    input  [3:0]    WIDTH;           // Duty Ratio (0 - 15)
    input          CLK, RST_B;       // Clock, Reset
    output         OUT;             // Blinking PWM Output

    wire          dout, pout;

    // Structure of Modules
    DIV div1(.CLK(CLK), .RST_B(RST_B), .DOUT(dout));
    PWM pwm1(.WIDTH(WIDTH), .CLK(dout), .RST_B(RST_B), .POUT(pout));
    BLNK blnk1(.IN(pout), .RST_B(RST_B), .OUT(OUT));

endmodule
```

Divider

```
module DIV(CLK, RST_B, DOUT);

    parameter          NDIV = 15;    // Bit of Divider
    input              CLK, RST_B;    // Clock, Reset
    output             DOUT;          // PWM Output
    reg                DOUT;
    reg [NDIV-1:0]     div;

    always @(posedge CLK or negedge RST_B) begin
        if(!RST_B) begin
            div <= 0;
            DOUT <= 1'b0;
        end
        else begin
            div <= div + 1;
            DOUT <= (&div) ? ~DOUT : DOUT;
        end
    end
end
endmodule
```

Pulse width modulator

```
module PWM(WIDTH, CLK, RST_B, POUT);

    input  [3:0]    WIDTH;    // Pulse width
    input          CLK, RST_B; // Clock, Reset
    output         POUT;      // PWM Output
    reg           POUT;
    reg  [3:0]    count;

    always @(posedge CLK or negedge RST_B) begin
        if(!RST_B) begin
            POUT <= 1'b0;
            count <= 4'b0000;
        end
        else begin
            count <= count + 4'b0001;
            POUT <= (WIDTH >= count);
        end
    end
end
endmodule
```

Blinking

```
module BLNK(IN, RST_B, OUT);

    parameter Nper = 256; // Period of blinking
    input    IN, RST_B; // Input, Reset
    output   OUT;       // Blinking Output
    reg [8:0] cnt;

    always @(posedge IN or negedge RST_B) begin
        if(!RST_B) begin
            cnt <= 9'b000000000;
        end
        else begin
            cnt <= cnt + 9'b000000001;
        end
    end

    assign OUT = (cnt < Nper) ? IN : 1'b0;
endmodule
```

Test bench

```
`timescale 1ns / 1ns
module tb_led;
    // Inputs
    reg [3:0]      width;
    reg           clk;
    reg           rst_b;
    // Outputs
    wire          out;

    // Half cycle of clock
    parameter hf_cycle = 1;
    parameter Nstep = 1000000000;
    parameter DUTY = 5;
    integer i, j;

    // Instantiate the Unit Under Test
    LED uut (.WIDTH(width), .CLK(clk), .RST_B(rst_b), .OUT(out));
```

Test bench (cont'd)

```
initial begin
// Initialize Inputs
width <= 4'b0000;
rst_b <= 1'b0;

// Wait 100 ns for global reset
#(2*hf_cycle) rst_b <= 1'b1;


// pulse width modulation
for (j = 0; j < Nstep/(64*65536); i = i + 1)
    #(64*65536*hf_cycle) width <= width + 1'b0001;
end
// Clock Generation
initial begin
    clk <= 1'b0;
    for (i = 0; i < Nstep; i = i + 1)
        #(hf_cycle) clk <= ~clk;
    $finish;
end
endmodule
```

Summary

- A logic circuit can be synthesized from HDL code written in RTL.
- The test bench can be described by HDL code in any level of detail by using # delay time.
 - Type in RTL: wire, reg, and integer
 - Assignment in RTL: assign statement or <=
 - Synchronization with clock edge: always @(posedge or negedge)
 - Do not use blocking assignment in RTL to exclude the timing ambiguity.
- Structural description can be used for the hierarchal design.

Appendix 1a

1. Edit and save your Verilog HDL file.
2. Start Modelsim.
3. Menu - [File] - [Change Directory...], and choose your working directory in which your Verilog HDL file is saved.
4. Click the Compile button on the toolbar and choose all Verilog HDL files to be simulated.
5. Click the Compile button on the open file selection dialog.

 

Appendix 1b

6. Confirm the error message in the Transcript window.
7. If you find the message "Errors: 0, Warnings: 0", click Done button the file selection dialog.
8. Click the Simulation button.
9. Choose [work] - Your test bench file and click the OK button on "Start Simulation" form.
10. Choose the name of the instance of DUT in the "Default" column in the left side.
11. Choose the signal names monitored in the "Objects" column in the right side and right-click.
12. In the pop-up menu, choose "Add Wave" to add the list of the signal names.
13. The waveform window is opened with the tracks of signals.
14. Click the "Run-All" button to start the simulation.
15. The simulation result is shown in the waveform window