
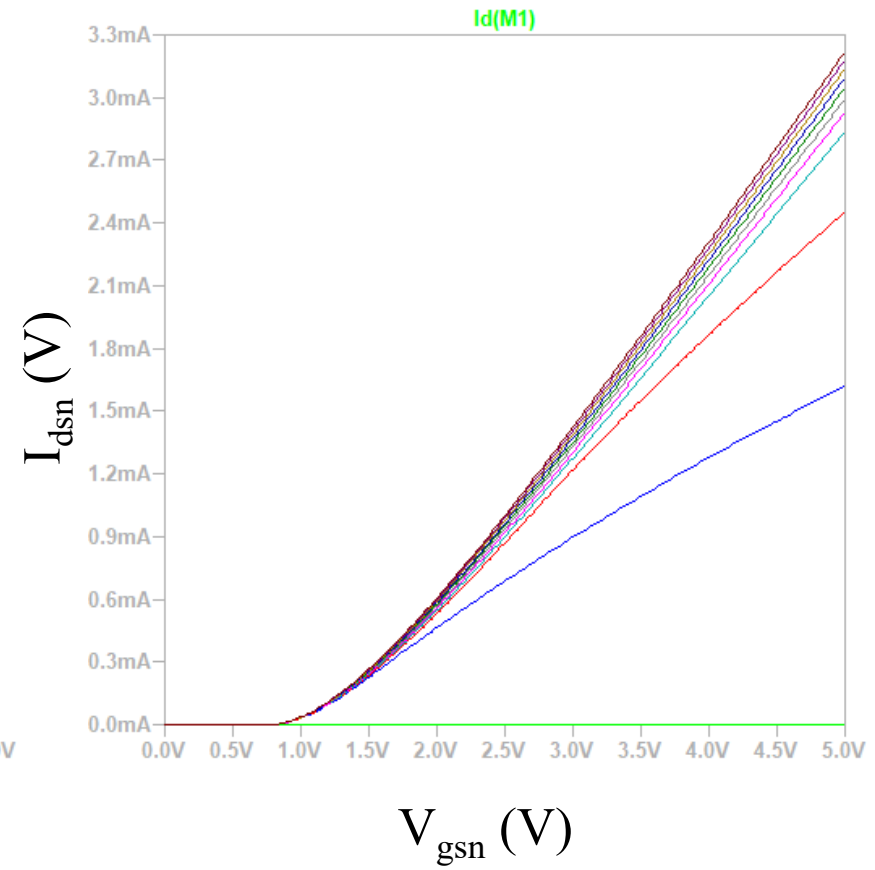


Lab. 01 Example solution

# **INSTALLATION OF CIRCUIT SIMULATOR**

# DC analysis of n-ch MOSFET

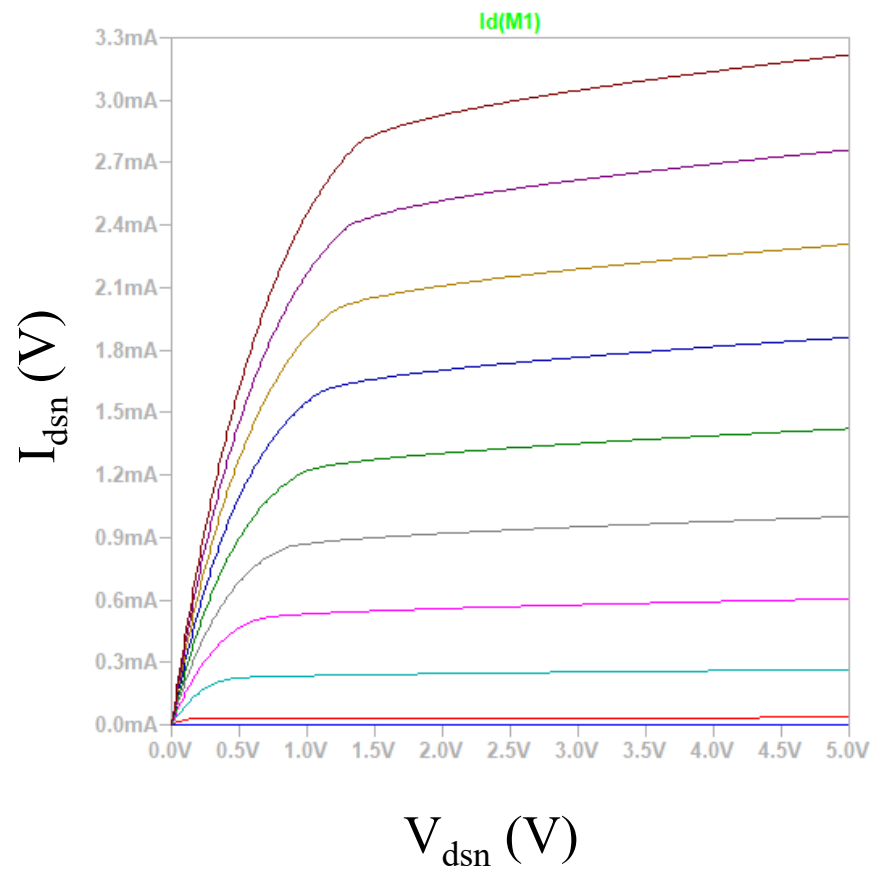

# DC analysis of p-ch MOSFET

