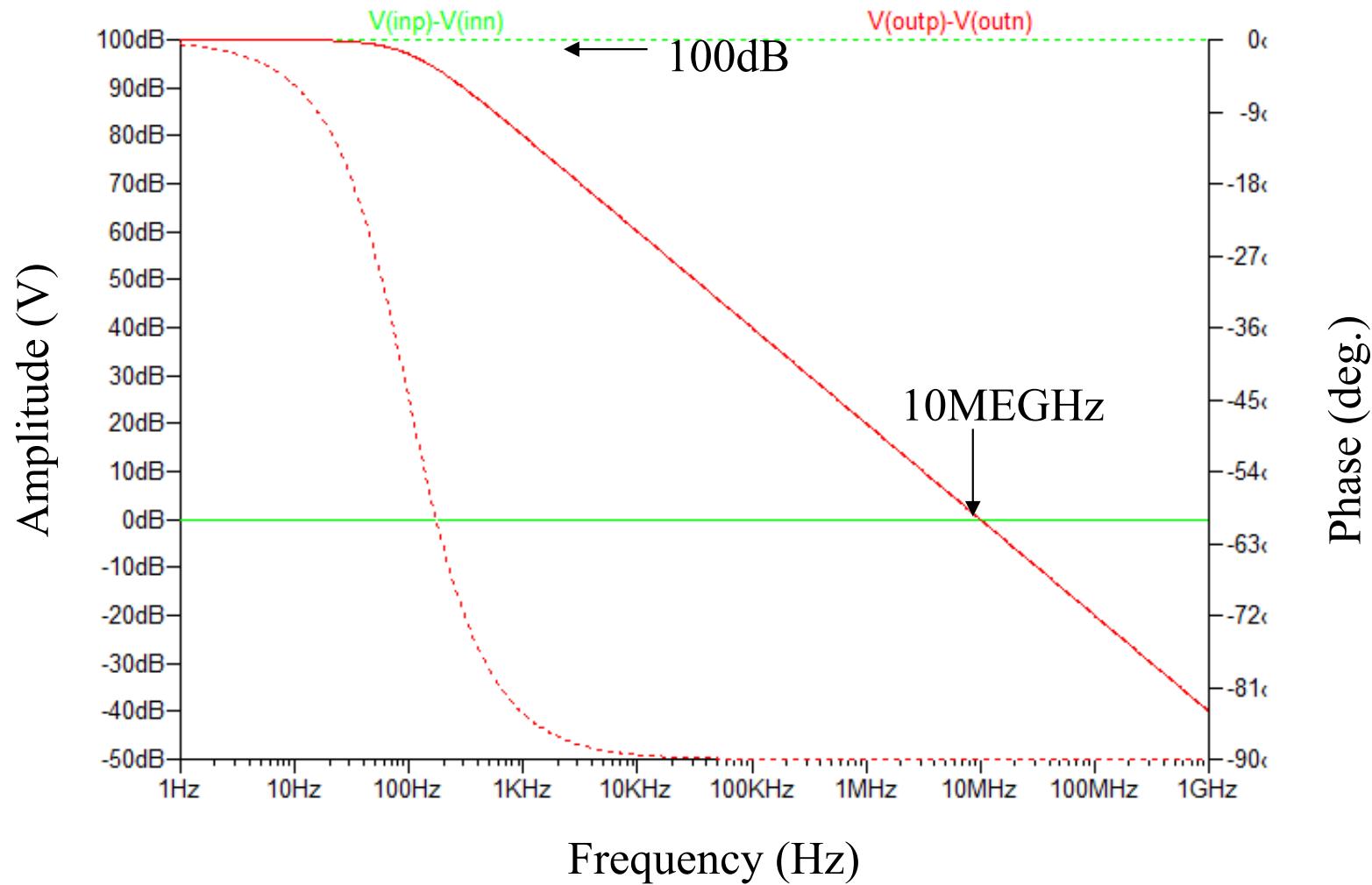



Lab. 03 Example solution

CHARACTERIZATION OF ANALOG INTEGRATORS


AC response of behavioral model of full-differential OPA



AC response of CAI with behavioral model

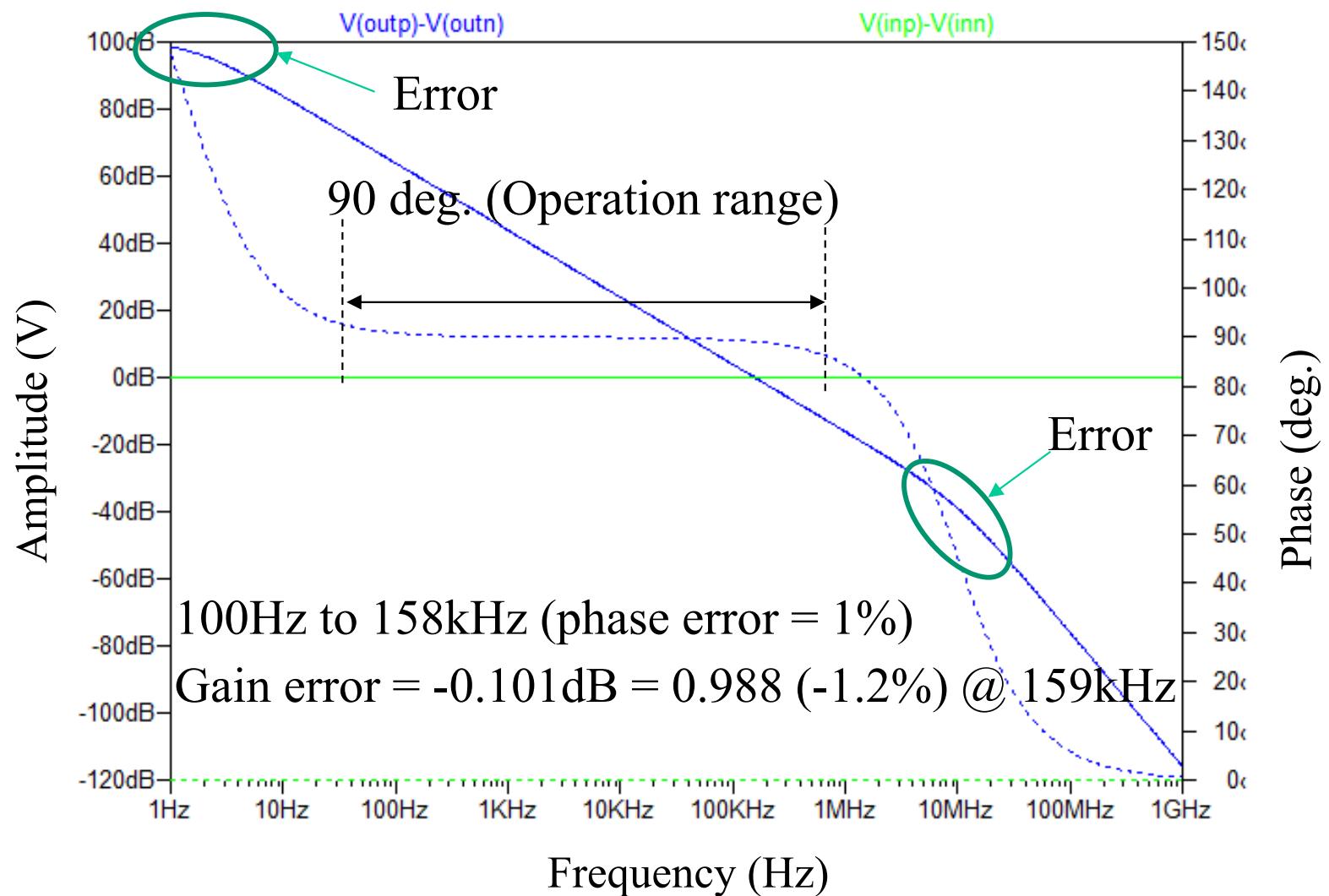

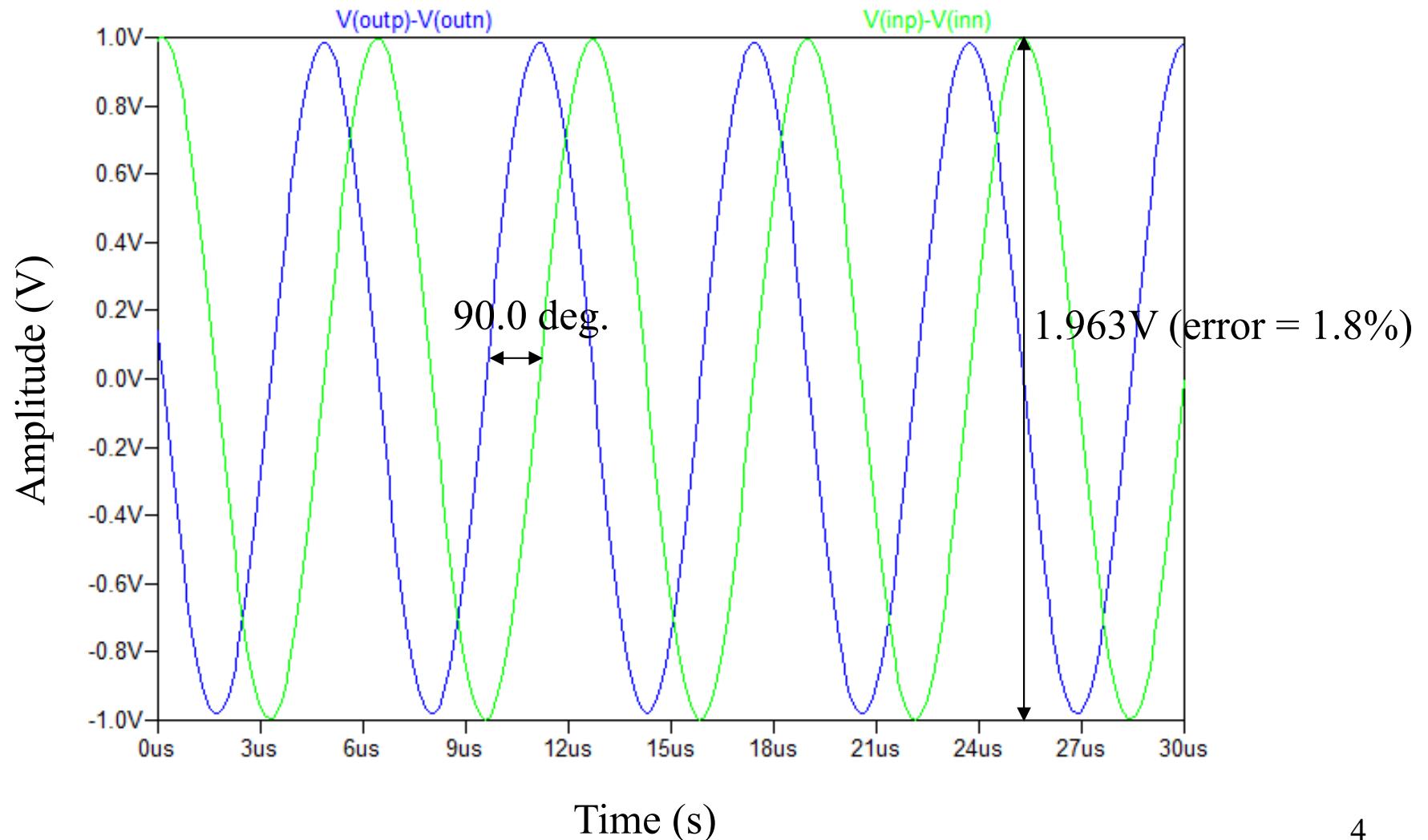Transient response of CAI with behavioral model



Transient response of DAI with behavioral model

