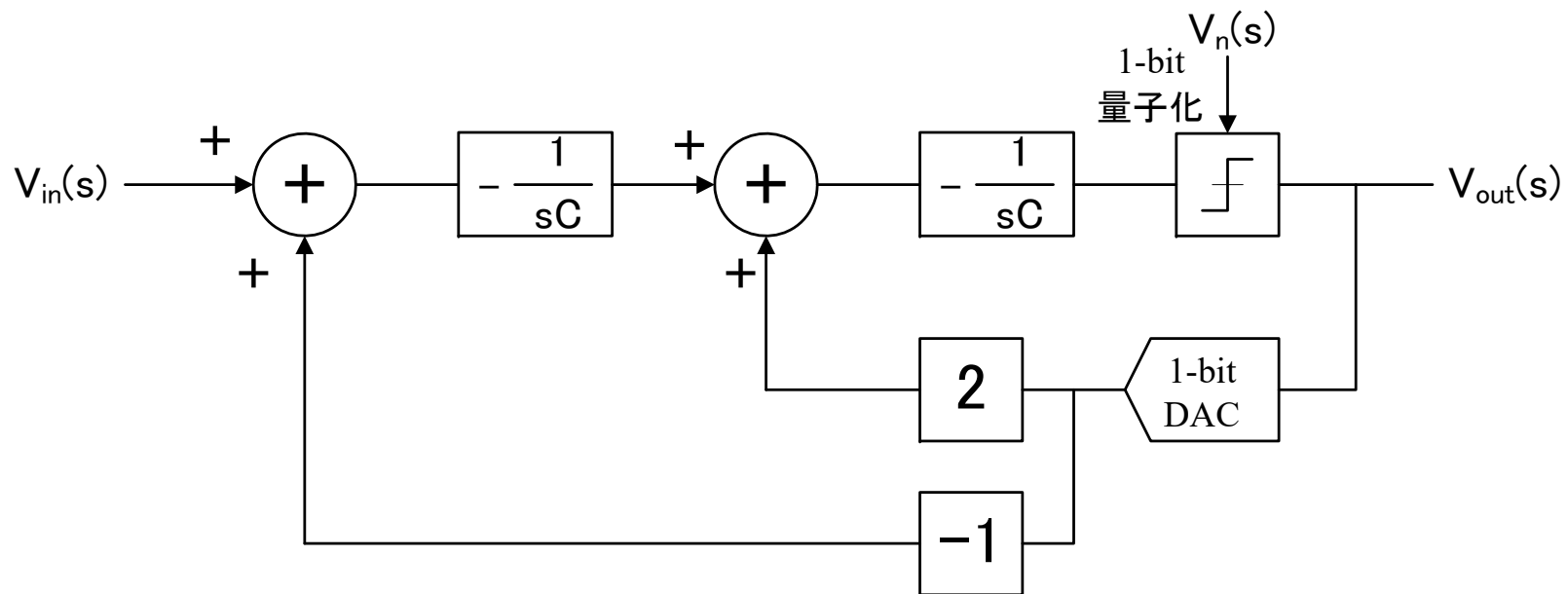


Problems 04

# **DELTA-SIGMA MODULATORS**


# Problem 1

1. Assuming that the delay time of quantizer is 0s, find the transfer functions  $H_s(s) = V_{out}(s)/V_{in}(s)$ , ( $V_n(s) = 0$ ) and  $H_n(s) = V_{out}(s)/V_n(s)$ , ( $V_{in}(s) = 0$ ).
2. Find the poles and zeros of  $H_s(s)$  and  $H_n(s)$ , respectively.
3. What type filters (LPF, BPF, HPF) are the frequency responses of  $H_s(s)$  and  $H_n(s)$  classified as?



# Problem 2

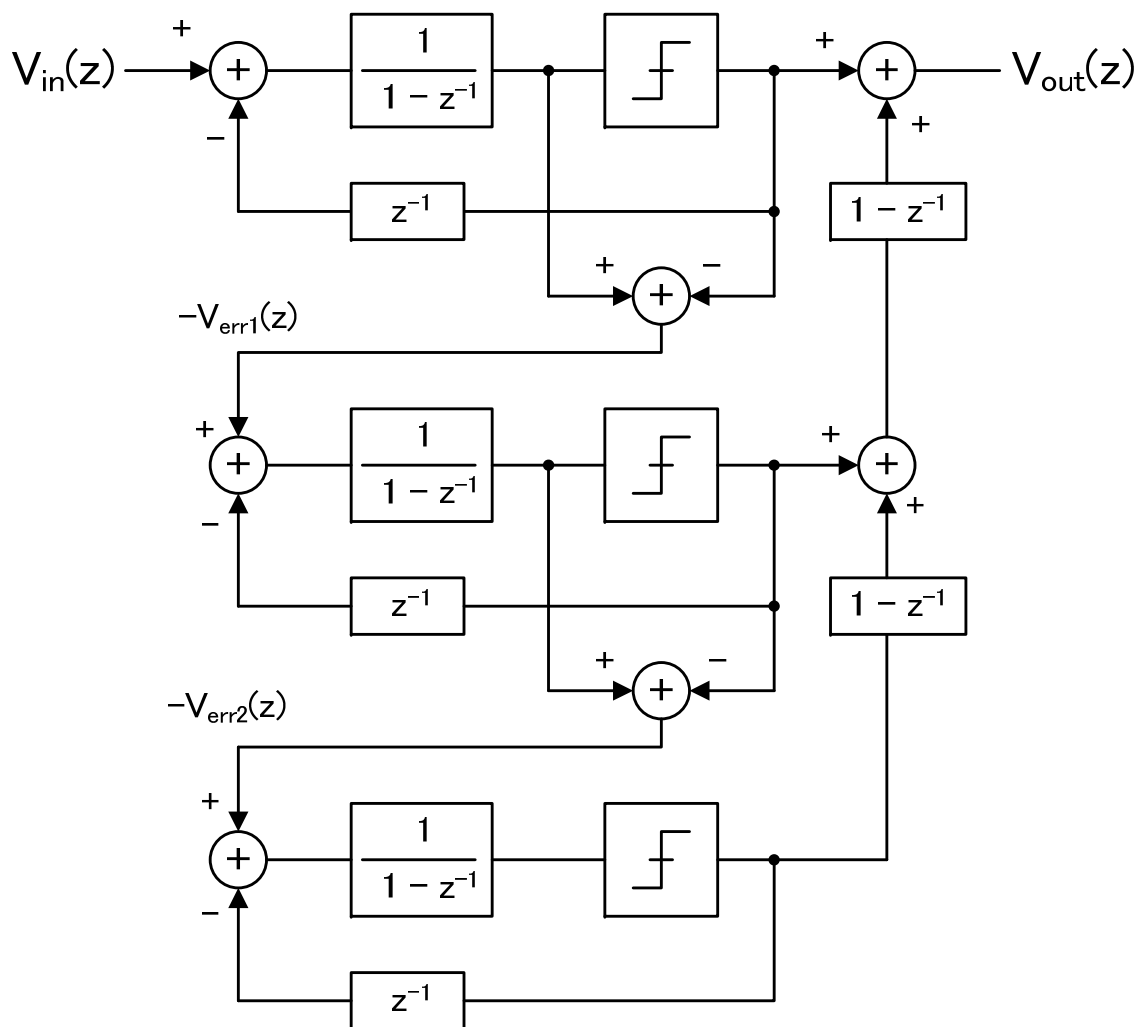- (1) Find the transfer function. Also show the calculation process.



# Problem 3

1. Find the transfer function. Also show the calculation process.

