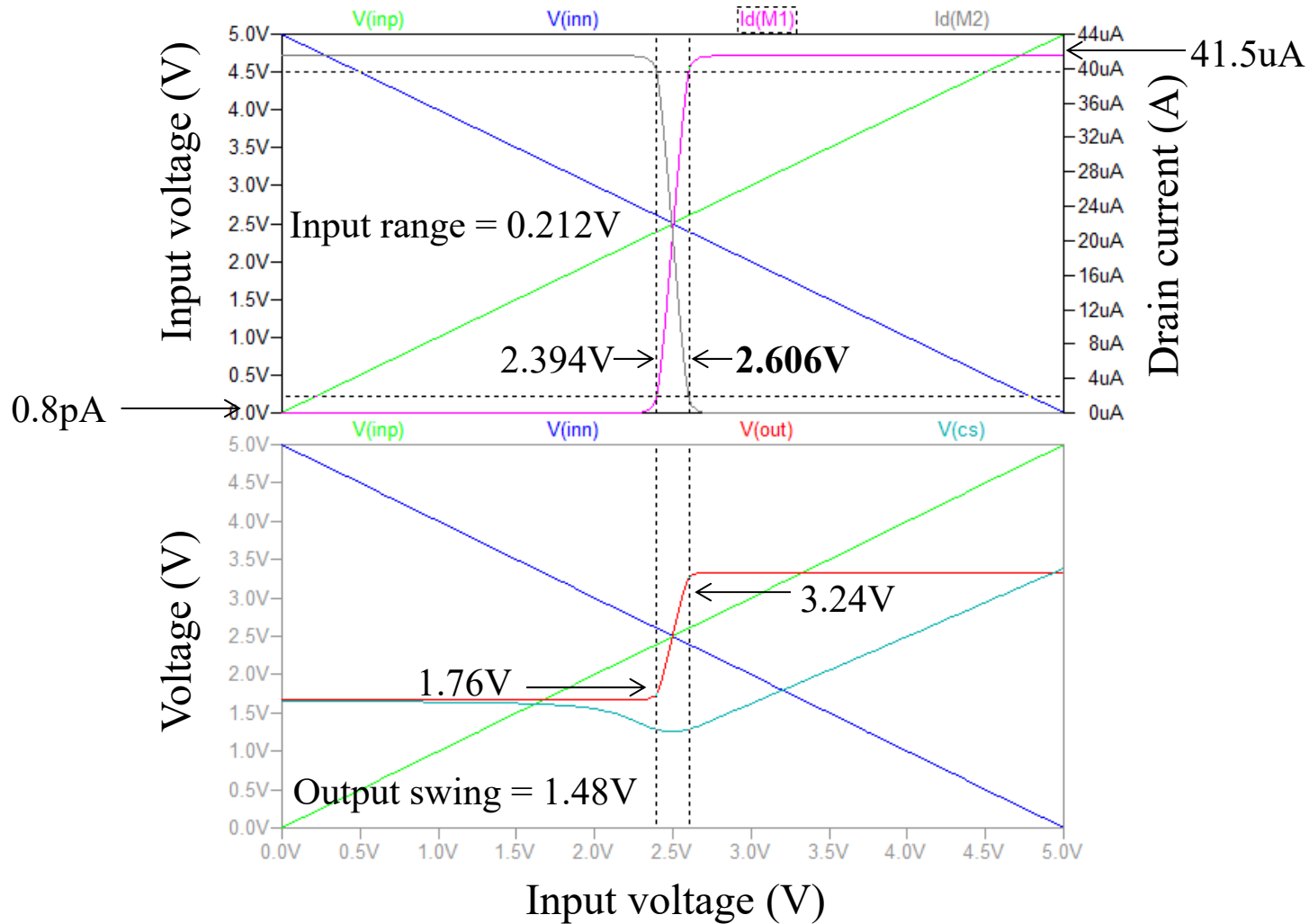



Lab. 11 Example solution

CHARACTERIZATION OF DIFFERENTIAL AMPLIFIER


DC characteristic



AC response

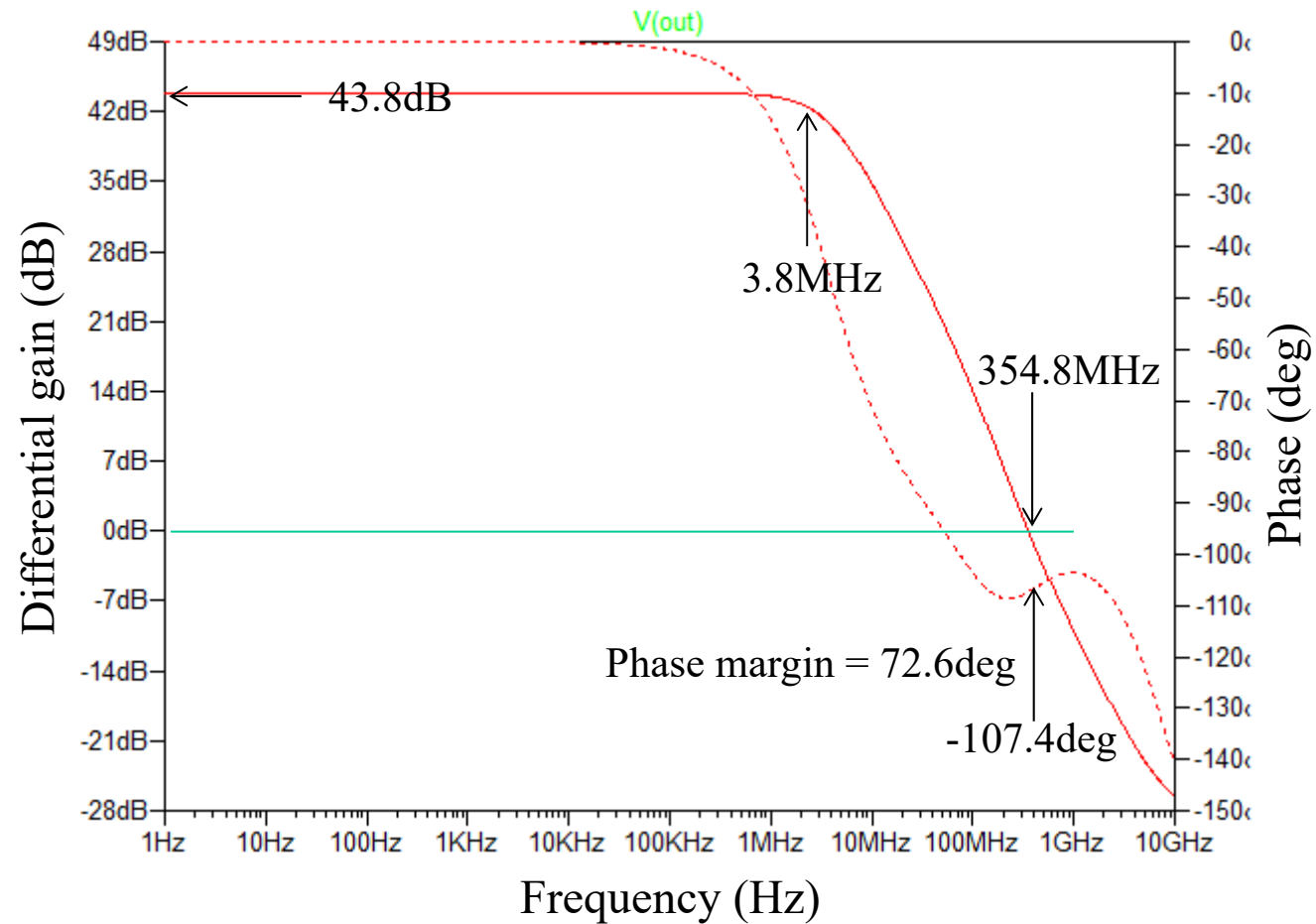

TRAN response

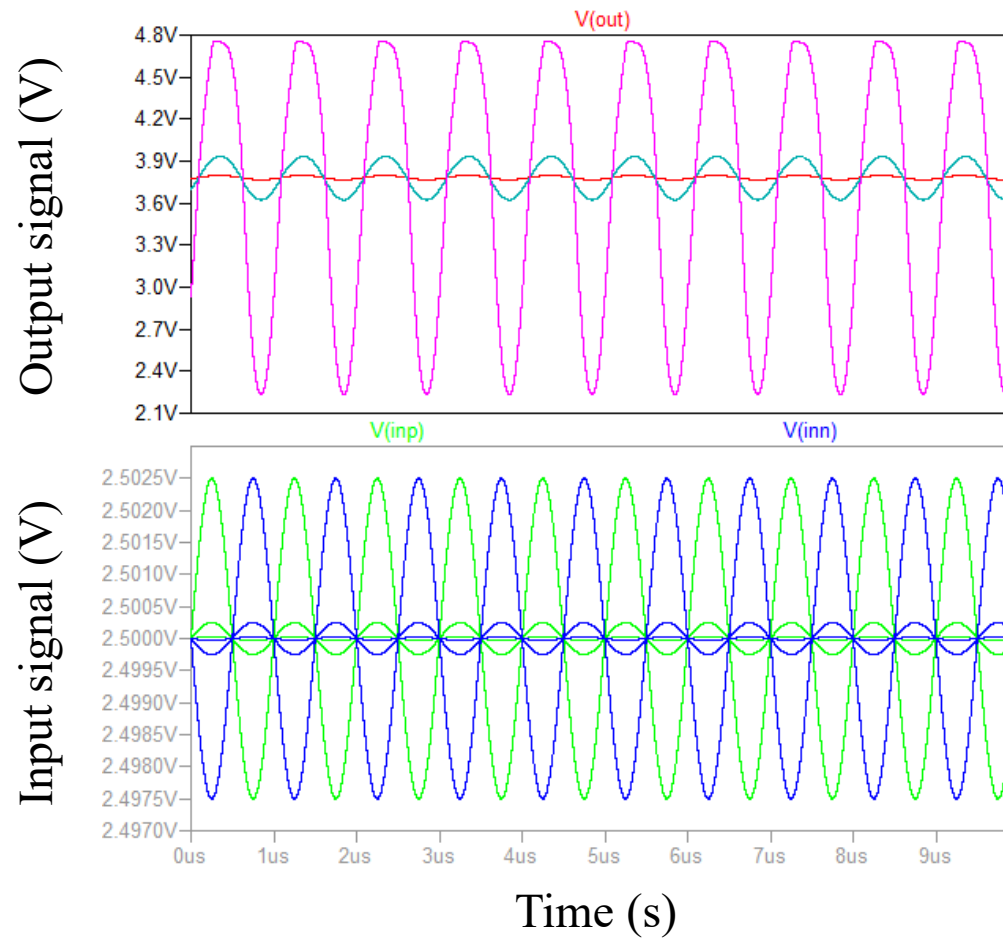

FFT

