

# 3.1 Design of logic functions

Basic structure of combinational logic  
and sequential logic

# Combinational Logic and Sequential Logic

- Combinational logic (組合せ回路)
  - The output value is a pure function of the present input only.
  - The function can be described by Boolean Expressions or a truth table.
  - The circuit is implemented by a wired logic or a LUT ( Look-up Table).
- Sequential logic (順序回路)
  - The output depends not only on the present value of its input signals but on the current state that is a result of the sequence of past input
  - The function can be described by a state transition diagram or a characteristic table.
  - The circuit is implemented by a combinational logic and registers (\*).

\* Register: A register is a logic circuit to storages the data for a clock cycle.

# Implementation of combinational logic

Boolean Expression  $\longleftrightarrow$

$$x = \overline{a \cdot b}$$


$$y = a + b$$



Truth table

a	b	x	y
0	0	1	1
0	1	1	0
1	0	1	0
1	1	0	0


Wired logic

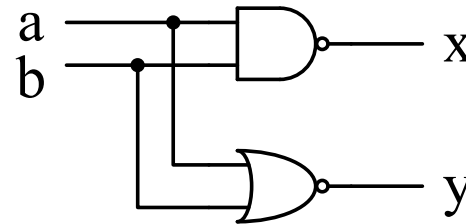

||

LUT (Look-up Table)

(ab) address	Memory								
00	1	1	DC	DC	DC	DC	DC	DC	
01	1	0	DC	DC	DC	DC	DC	DC	
10	1	0	DC	DC	DC	DC	DC	DC	
11	0	0	DC	DC	DC	DC	DC	DC	
	data (x	y)	Unused						3


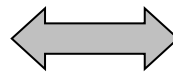


# Implementation of sequential logic

Characteristic table  
(特性表)

r	c	$q_1q_0(n+1)$
0	0	$q_1q_0(n)$
0	1	$q_1q_0(n) + "01"$
1	0	0 0
1	1	0 0

State Transition Diagram  
(状態遷移図)

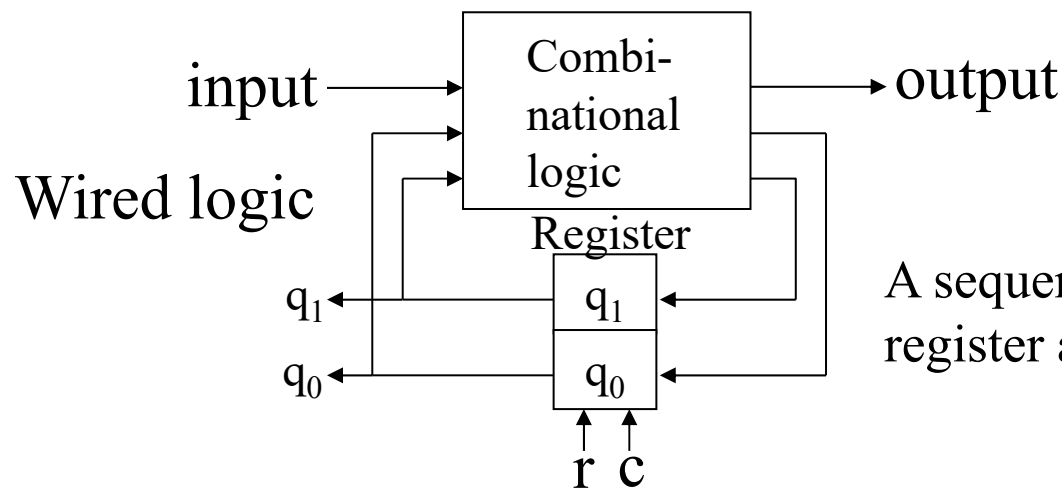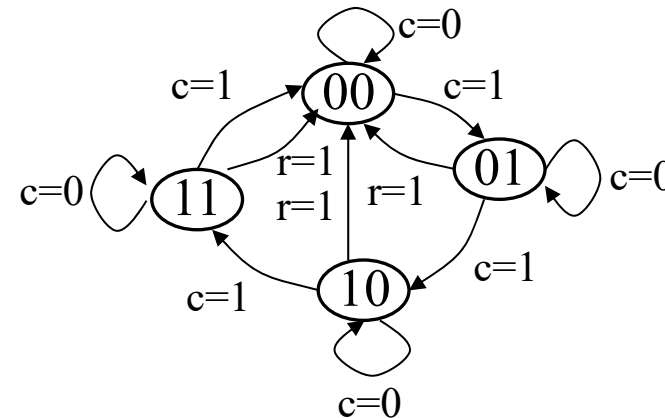

A sequential logic consists of a register and a combinational logic.