 


## 4.4 DC transfer characteristic


Noise margin and switching threshold  
voltage

# Transient of the operating point



# DC transfer characteristic

(直流伝達特性)

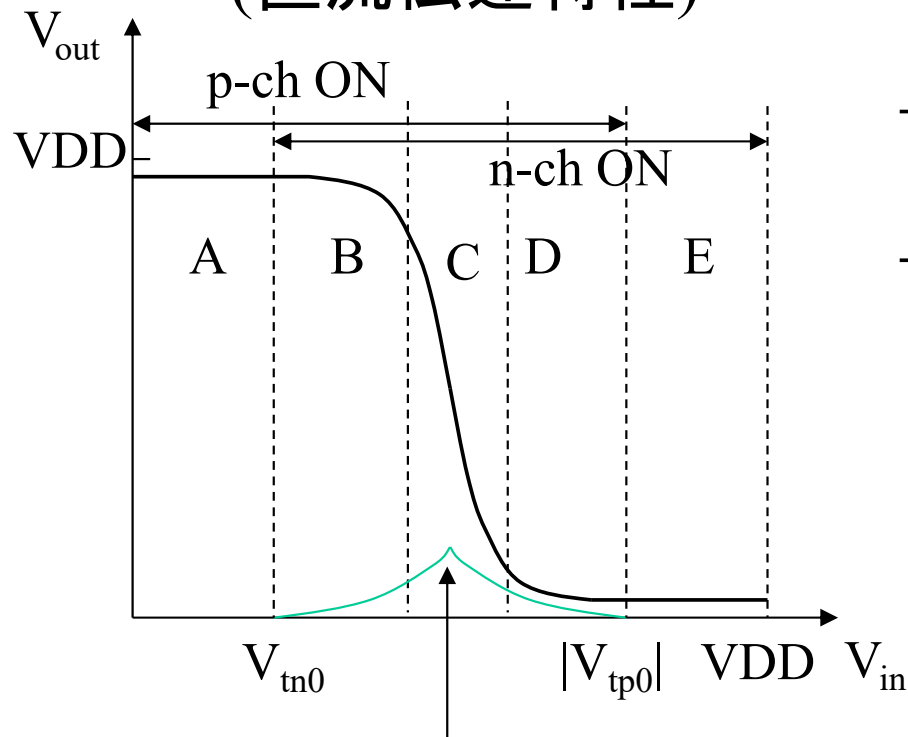

Input level	n-ch	p-ch
A	Sub-threshold	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Sub-threshold



$I_{dsn} = -I_{dsp}$  (Through-current)  
 The current flows for a moment of rising or falling edge of the input signal.

# Noise margin

Noise margin (雑音余裕度) =  $NM_H, NM_L$

- A large noise margin prevents errors.
- The noise margin of CMOS static logic is larger than that of other circuits.

DC transfer characteristic

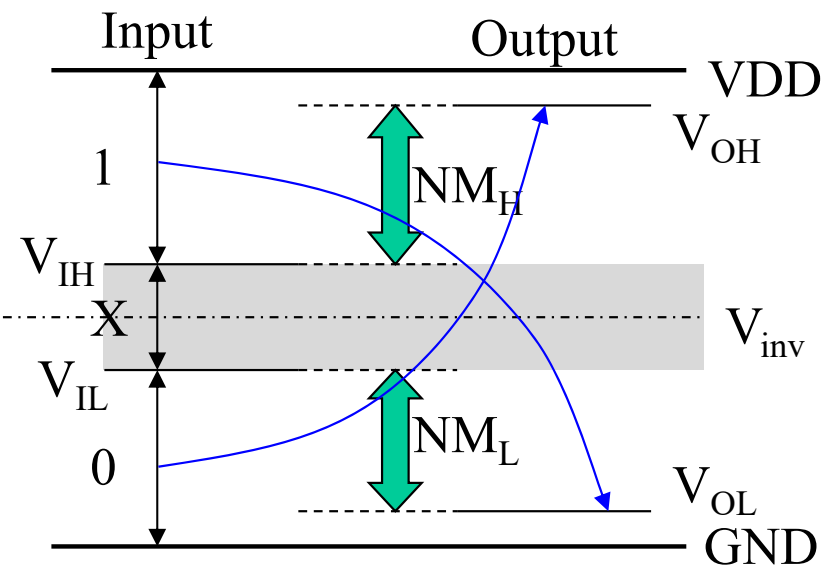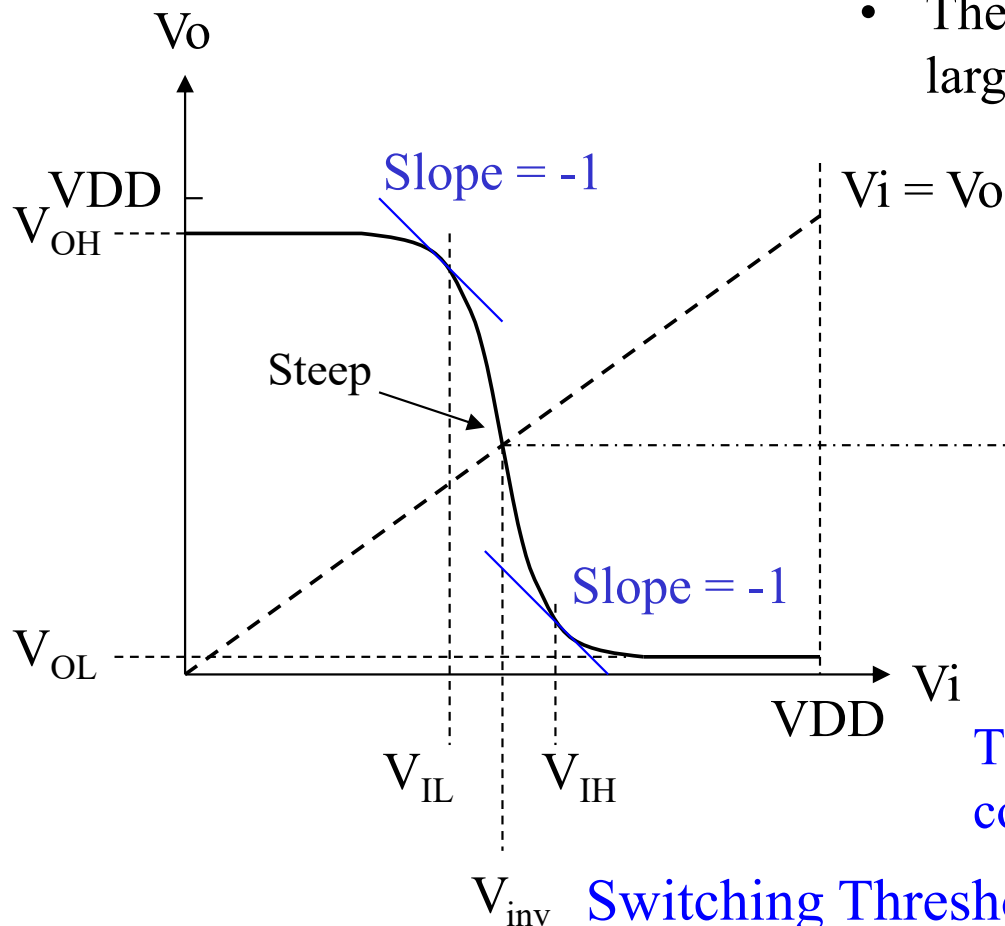


The amplitude error of the input voltage is corrected by the voltage gain of logic gates.

Switching Threshold Voltage

(ゲートのスイッチング閾値電圧)
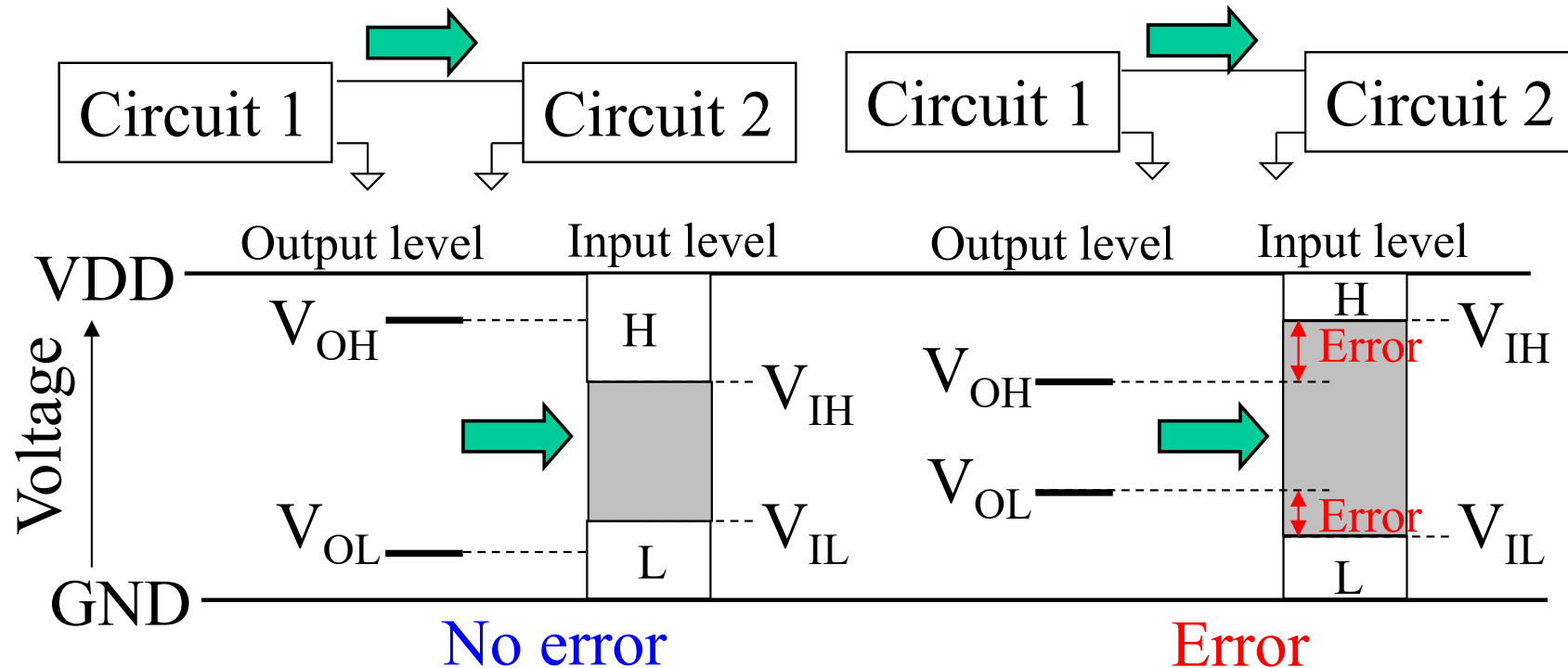
# Threshold level

- The values of  $V_{IH}$ ,  $V_{IL}$ ,  $V_{OH}$ , and  $V_{OL}$  are called threshold levels or IO levels.
- The threshold level depends the supply voltage and the circuit configuration. The circuits designed for the different threshold level cannot transfer the signals. (The level converter is required.)



# IO level

- The standard threshold levels of IO circuits (IO level) are defined to transfer the signals between the commercial LSIs.
- The circuits with the different threshold level cannot be directly connected.
  - Level converter
  - Open drain
- The IO level of FPGA is programmable.

Standard IO level	$V_{IL}(\text{max})$	$V_{IH}(\text{min})$	$V_{OL}(\text{typ})$	$V_{OH}(\text{typ})$
CMOS(5V), LVCMOS(3.3, 2.5, 1.8, 1.5, 1.2V)	$0.2 * V_{DD}$	$0.7 * V_{DD}$	0.4V	$V_{DD} - 0.8V$
TTL/LVTTL	0.8V	2.0V	0.35V	2.7V

TTL (Transistor-Transistor Logic): A type of bipolar transistor logic.

# $L_n, L_p, W_n, W_p,$ and $V_{inv}$

Gain coefficient  $\beta_n, \beta_p$

$$\begin{cases} \beta_n = \frac{W_n}{L_n} \mu_n C_o \\ \beta_p = \frac{W_p}{L_p} \mu_p C_o \end{cases}$$

Usually, the manufacture controls the threshold voltage of MOSFET in order that  $V_{tn0} = -V_{tp0} = V_T$ .

$$I_{dsp} = -I_{dsn}$$

$$\frac{\beta_p}{2} (V_{inv} - VDD + V_T)^2 = \frac{\beta_n}{2} (V_{inv} - V_T)^2$$




$$VDD - \left( 1 \mp \sqrt{\frac{\beta_n}{\beta_p}} \right) V_T$$

Switching threshold of inverter

$$V_{inv} = \frac{VDD - \left( 1 \mp \sqrt{\frac{\beta_n}{\beta_p}} \right) V_T}{1 \pm \sqrt{\frac{\beta_n}{\beta_p}}}$$
 
# Design of gate switching threshold $V_{inv}$

From the previous slide,  $\sqrt{\frac{\beta_n}{\beta_p}} = 1$  When  $\beta_n = \beta_p$ ,  $V_{inv} = \frac{VDD}{2}$



The output level  $V_{OH}$  and  $V_{OL}$  is fixed.

When  $V_{inv} = VDD/2$ ,  $NM_H$  and  $NM_L$  become equivalent. (The small noise margin causes errors.)



# Optimization of $L_n$ , $L_p$ , $W_n$ , $W_p$ -1

$$\beta_n = \beta_p$$

$$\frac{W_n}{L_n} \mu_n C_O = \frac{W_p}{L_p} \mu_p C_O$$

$$\boxed{\frac{W_n}{L_n} \mu_n = \frac{W_p}{L_p} \mu_p}$$

← The capacitance of gate oxide of n-ch MOSFET is exactly equals to that of p-ch MOSFET.

$$\frac{W_n}{L_n} : \frac{W_p}{L_p} = 1 : 1.5 \sim 3.0$$

← The mobility  $\mu_n$  and  $\mu_p$  depends on manufacturing process.

# Optimization of $L_n$ , $L_p$ , $W_n$ , $W_p$ -2

The gate length  $L_n$  and  $L_p$  is normally set to the minimum size of the technology, because the operation speed of MOSFET with smaller  $L_n$ ,  $L_p$  is larger.




$$\frac{W_n}{L_n} \mu_n = \frac{W_p}{L_p} \mu_p$$

When  $L_n = L_p$

$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = 1.5 \sim 3.0 \quad \Rightarrow$$


In the practical circuit design, simulate the logic circuit under the condition of  $W_p/W_n = 2$ , then adjust  $W_p/W_n$  in order that the switching threshold equals to  $V_{DD}/2$ .
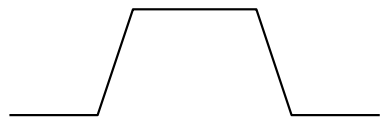
# Waveform of output signal


Condition	$V_{inv}$	Speed of rising edge	Speed of falling edge	Output wave form
$\beta_n = \beta_p$	$= V_{DD}/2$	Medium	Medium	
$\beta_n > \beta_p$	$< V_{DD}/2$	Slow	Fast	
$\beta_n < \beta_p$	$> V_{DD}/2$	Fast	Slow	

When  $V_{inv} = V_{DD}/2$ , NM is maximized, and the rising speed and the falling speed is balanced.
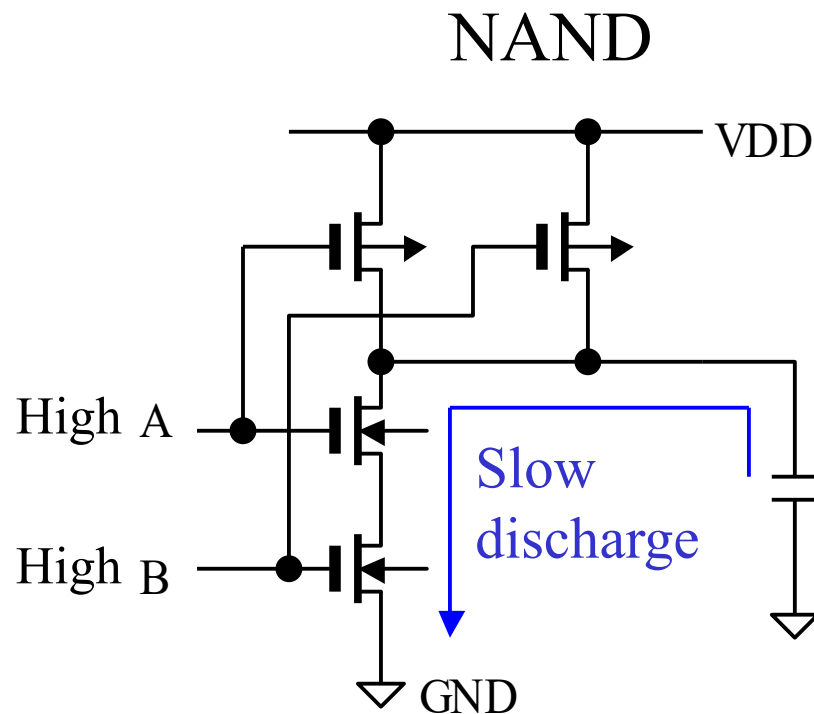
# DC transfer characteristic of multi-input gates




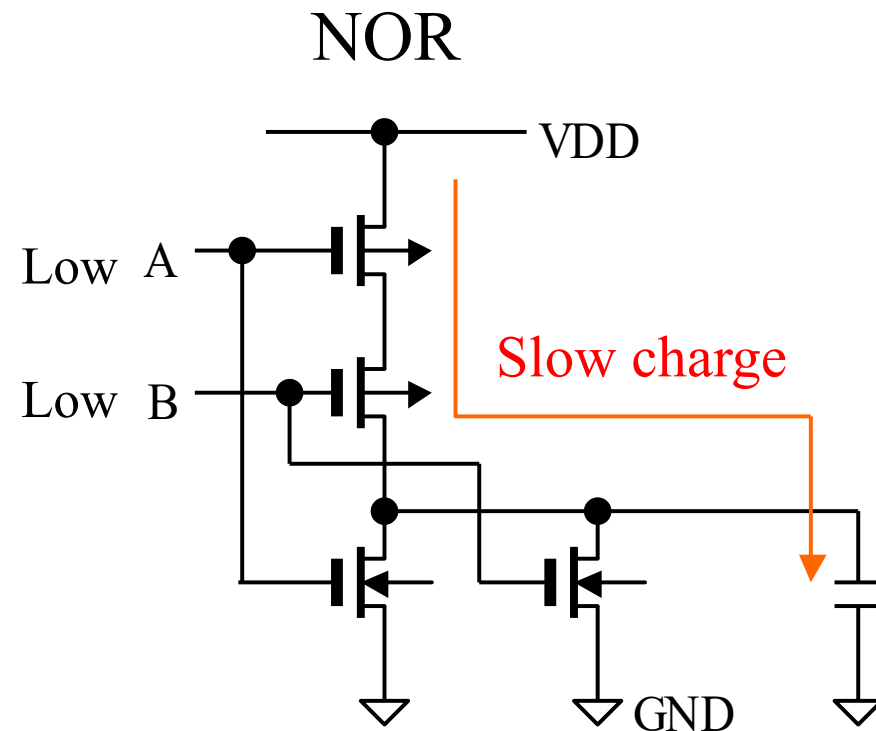To improve the discharge speed,  $W_n$  must be larger than  $W_p$  of PUN transistors.



To improve the charge speed,  $W_p$  must be larger than  $W_n$  of PDN transistors.


# Gate width of MOSFET

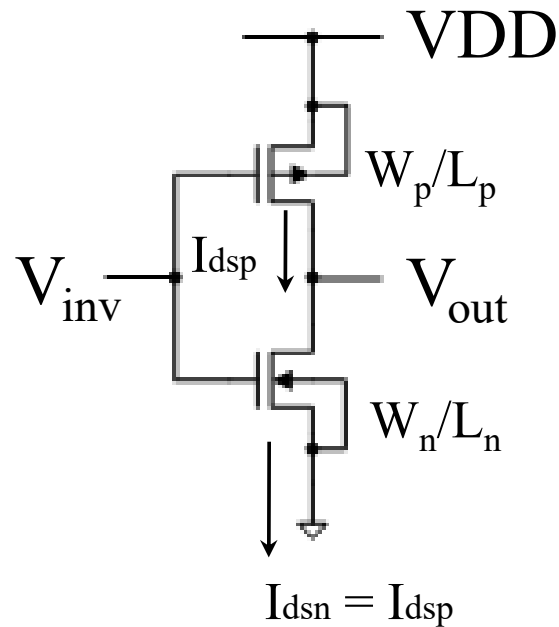

When  $\beta_n = \beta_p$ ,

$$V_{inv} = VDD/2.$$
 
$$\frac{W_n}{L_n} \mu_n = \frac{W_p}{L_p} \mu_p$$



When  $0.5\beta_n = 2\beta_p$ ,

$$V_{inv} = VDD/2.$$

$$\frac{W_n}{L_n} \mu_n = 2^2 \frac{W_p}{L_p} \mu_p$$

# Optimization of $L_n$ , $L_p$ , $W_n$ , $W_p$ of multi-input gates

When  $L_n = L_p$ ,  $\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = 1.5 \sim 3$  (for inverter)

Optimum value of  $W_p/W_n$


Number of inputs	1	2	N
Inverter	$\mu_n/\mu_p$		
NAND		$(\mu_n/\mu_p)/2^2$	$(\mu_n/\mu_p)/N^2$
NOR		$(\mu_n/\mu_p)2^2$	$(\mu_n/\mu_p)N^2$

# Number of parallel connections

The parameter  $M$  is defined as number of parallel connections.


$M$  is called a **multiplier** of MOSFET.

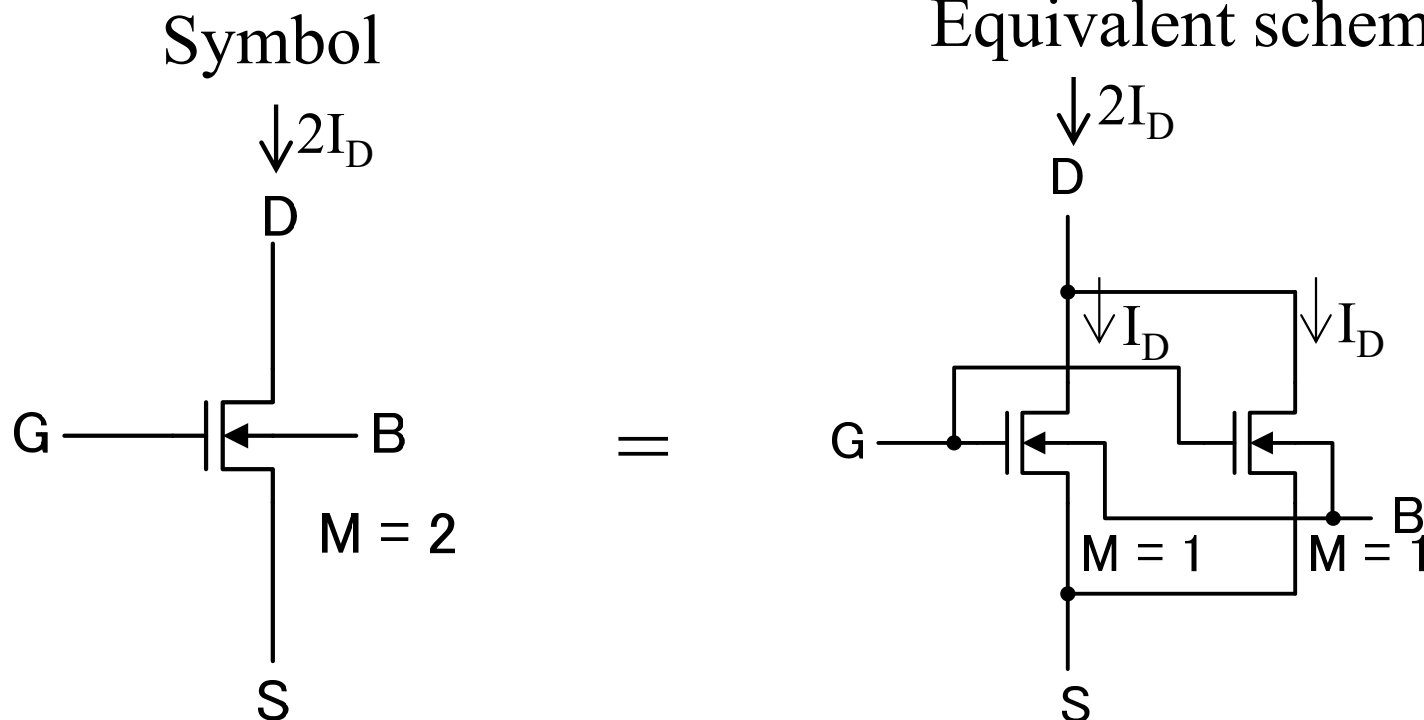When  $N$  is an input number of NAND, you may set a value of  $N^2$  as  $M$  of n-ch MOSFET.


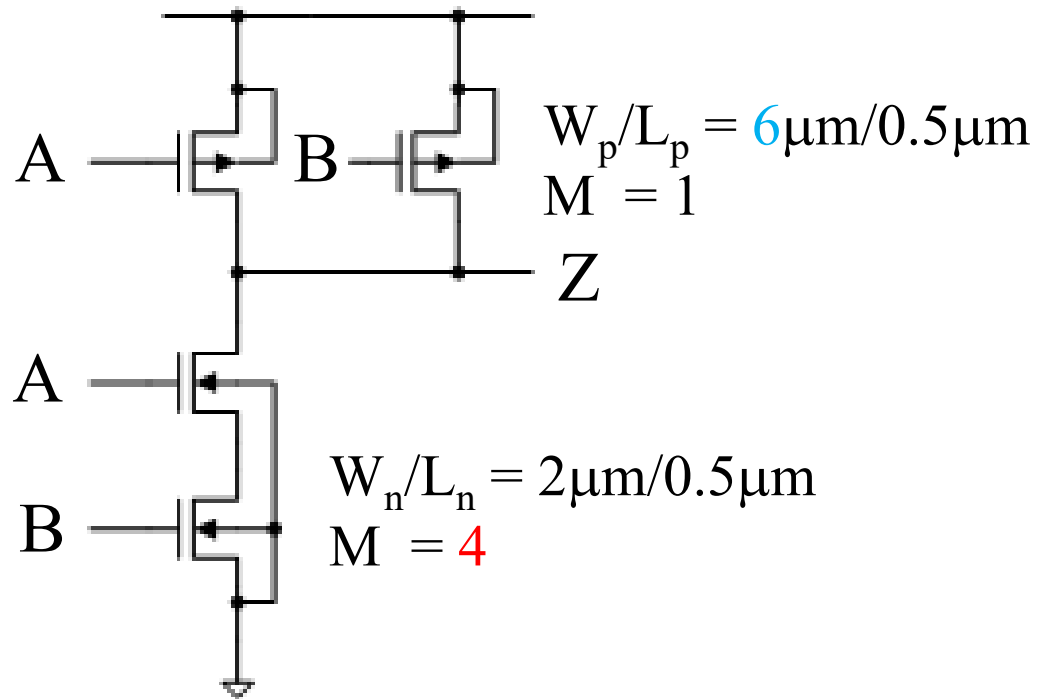
# Example of NAND design

$$L_n = L_p = 0.5\mu\text{m}, \mu_n/\mu_p = 3.0$$



$$0.5\beta_n = 2\beta_p$$

$$\beta_n = 2^2\beta_p$$

$$\mu_n C_o \frac{W_n}{L_n} = 2^2 \mu_p C_o \frac{W_p}{L_p}$$

$$\frac{\mu_n}{\mu_p} \frac{W_n}{L_n} = 2^2 \frac{W_p}{L_p} = M \frac{W_p}{L_p}$$