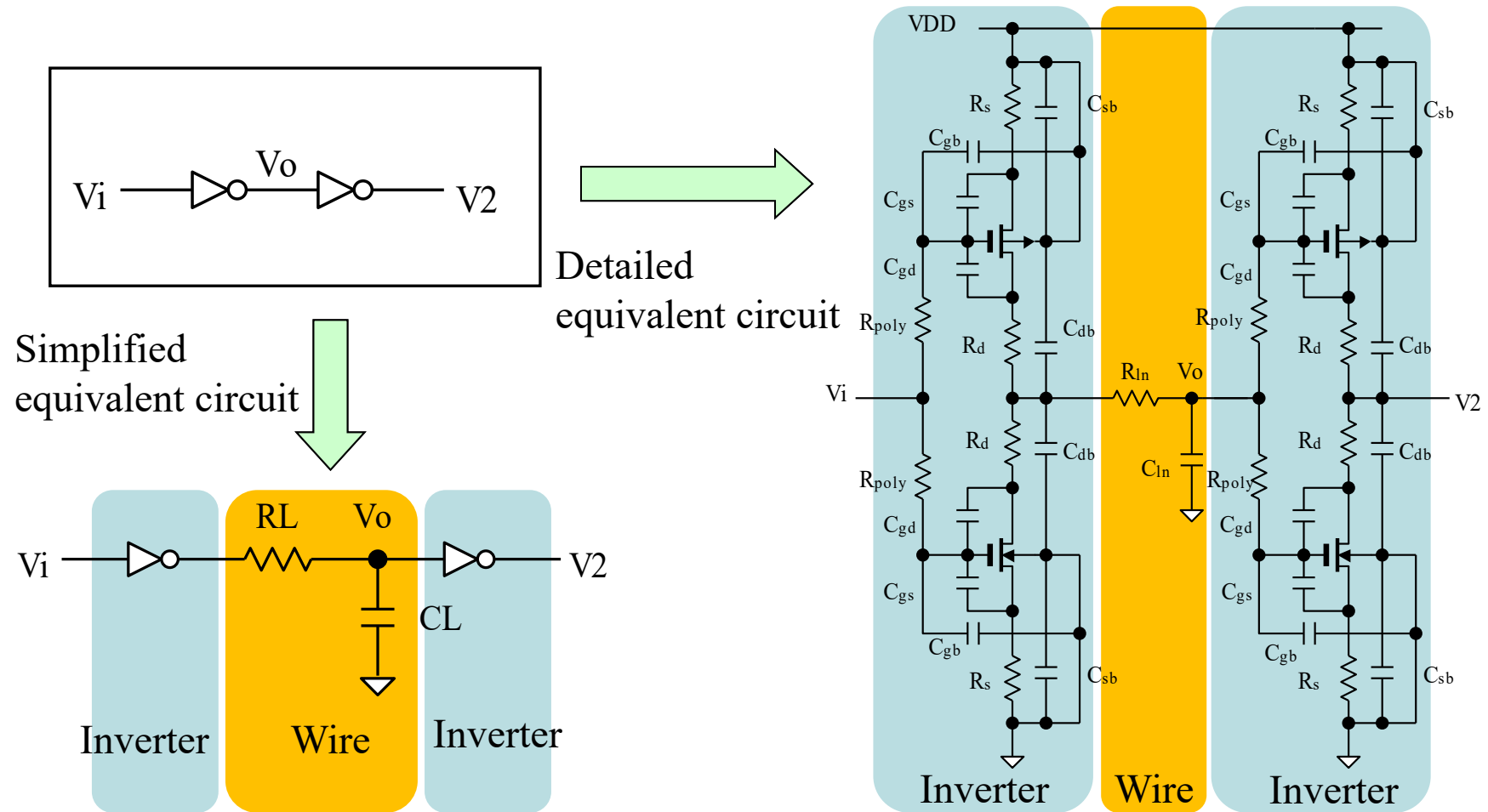


## 6.1 Operating speed

Analysis of delay time and clock frequency

## 6.1.1 Circuit characteristics considering parasitic elements



# Parasitic elements in LSI



Note: A MOSFET model includes the parasitic elements in the layout pattern.

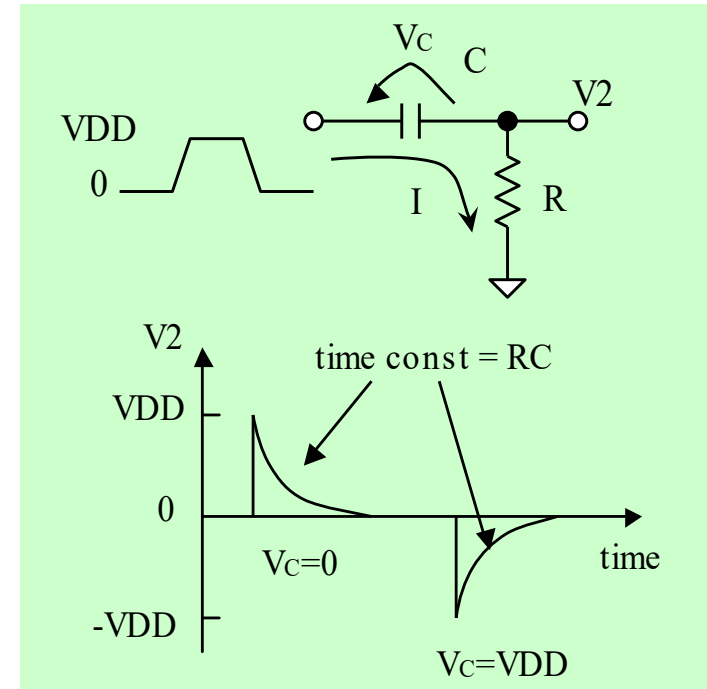 
# Transient response of parasitic elements

- A wire in LSI is modeled by parasitic resistances and parasitic capacitances.
  - Parasitic R and C depend on the length and the width of the wire.
  - A parasitic L must be considered in RF circuits.


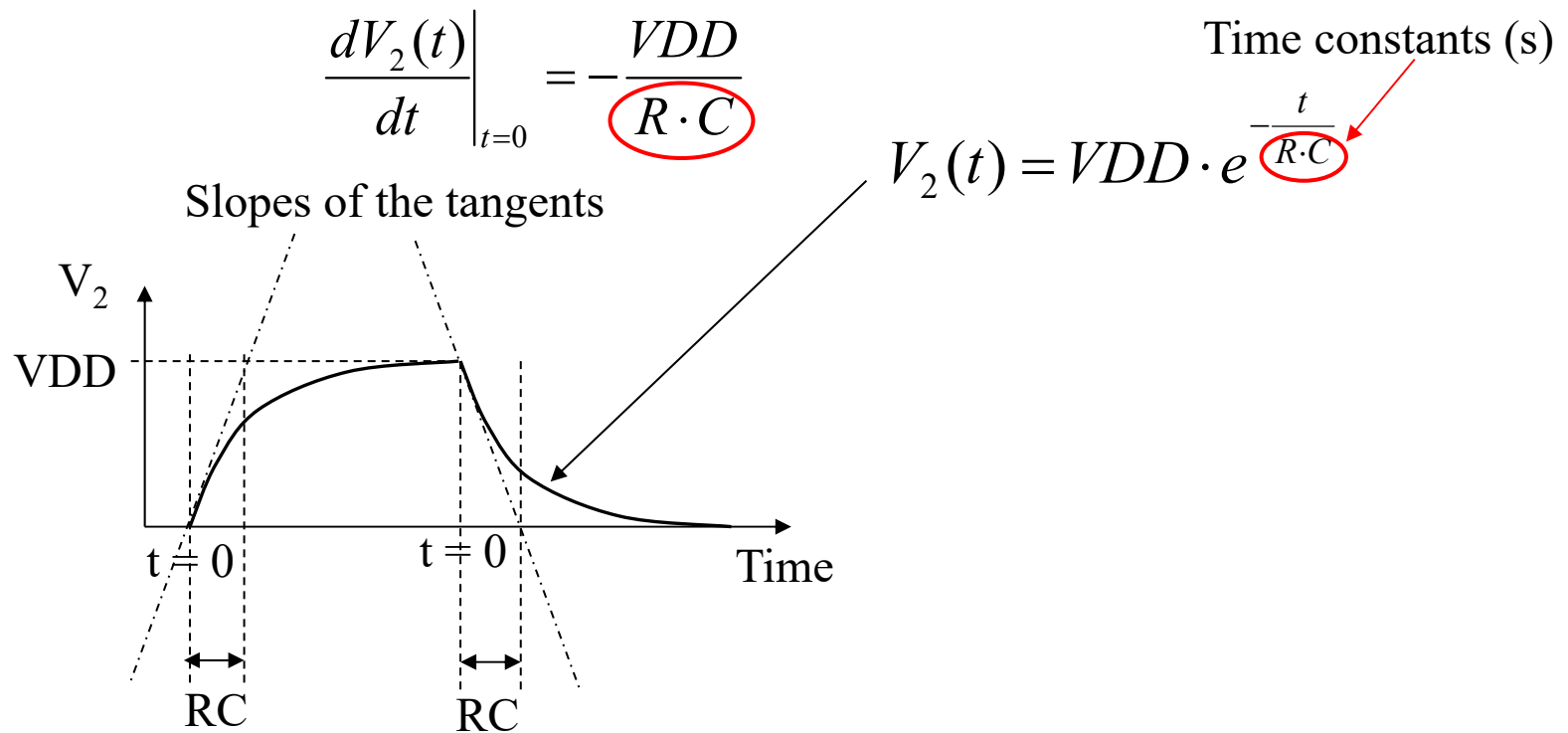
# Time constant

- The slopes of the tangents are increased with increasing the time constant  $RC$ . The  $R$  and  $C$  are the resistance and capacitance of the parasitic elements in the logic circuits.




## 6.1.2 Extraction of a parasitic resistance


The cause of the parasitic resistance
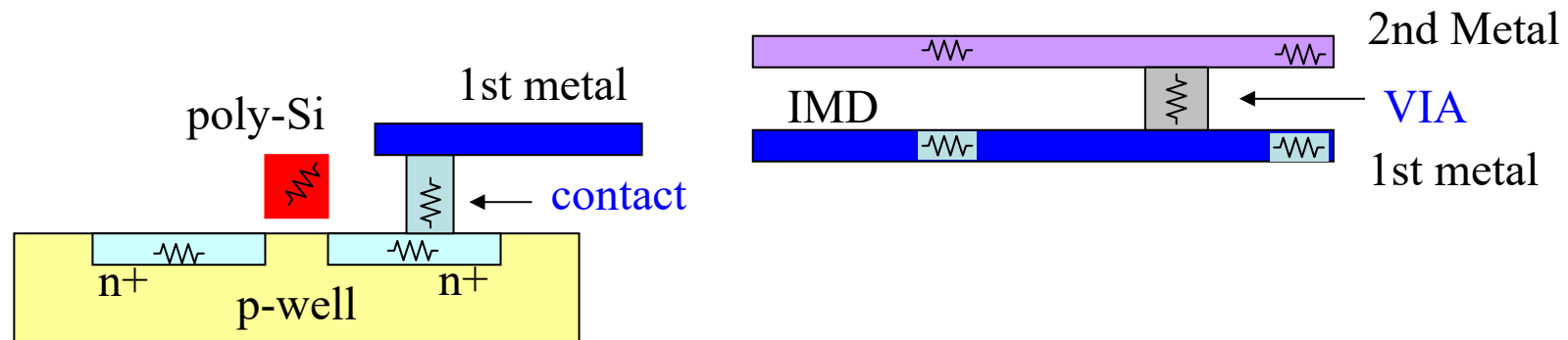
# Parasitic resistance

- Metal layer
- VIA
- Poly Si
- n-type Si layer and p-type Si layer
- Contact



# Estimation of resistance

 

$$R = \frac{\rho}{t} \frac{L}{W} = R_S \frac{L}{W}$$

$\rho$  (Wm) Resistivity

$R_S$  ( $\Omega/\square$ ) Sheet resistance

- The sheet resistance  $R_S$  of each layer is disclosed by the manufacture.
- The resistance  $R$  is estimated from the values of  $L$  and  $W$  in layout pattern.
- The measurement of  $R_S$  is easier than the measurement of  $\rho$ .





# Resistivity of Si

$$E(\text{V/m}) = \rho(\Omega\text{m})J(\text{A/m}^2)$$

The resistivity of Si depends on the donor or acceptor concentration.

  
The concentration dependence is called "Irvin curve".



Concentration of donors or acceptors ( $\text{cm}^{-3}$ )

# Measurement of sheet resistance

Top view

 


$$R = R_S \frac{L}{W} = R_S , \text{ when } L = W$$

The sheet resistance is measured by measuring the resistance at both sides.

[Note] The definition of the sheet resistance is different from the resistance, but the unit of  $R_S$  is the same as the unit of resistance ( $\Omega$ ). An unit  $\Omega/\square$  is used in order to distinguish the sheet resistance from the resistance.

# Examples of sheet resistance

- Parasitic resistance in 2-input NAND

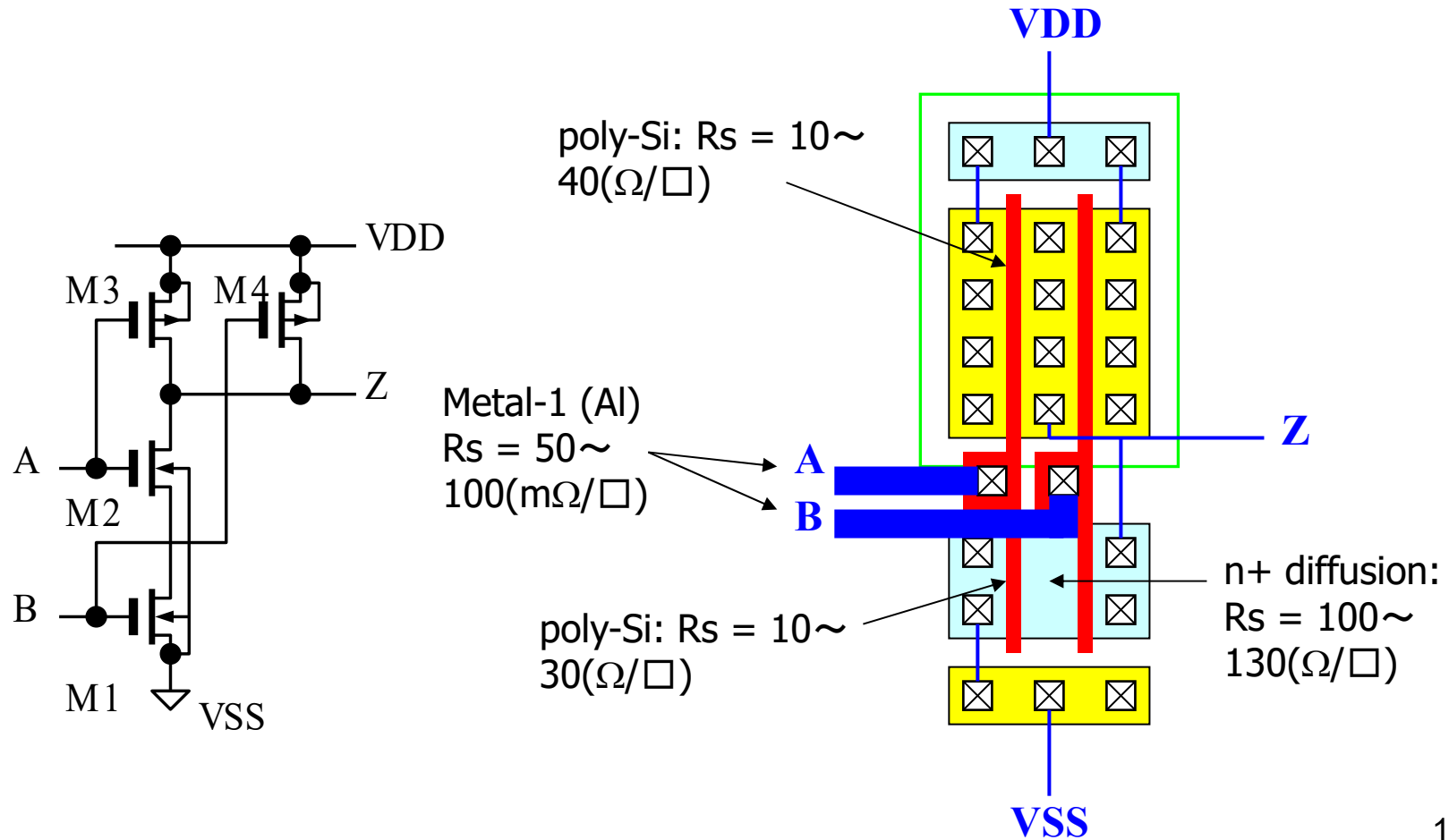

## 6.1.3 Extraction of a parasitic capacitance

The cause of the parasitic capacitance

# Parasitic capacitances in MOSFET

## 1. Gate oxide capacitance

$$C_{gc} = (L - L_{OV})WC_{OX}$$

$$C_{OX} = \epsilon_{SiO_2}\epsilon_0 \frac{1}{t_{ox}}$$


## 2. Overlap capacitance

$$C_{gso} = C_{gdo} = \frac{L_{OV}}{2}WC_{OX}$$
 
## 3. Depletion layer capacitance


$$C_d = \sqrt{\frac{qN_A\epsilon_{SiO_2}\epsilon_0}{2\phi_S}} \quad \phi_S \text{ and } C_d \text{ depend on the } V_{gs}.$$

$N_A$ : Impurity concentration in channel  
 $\phi_S$ : Surface potential of MOS interface



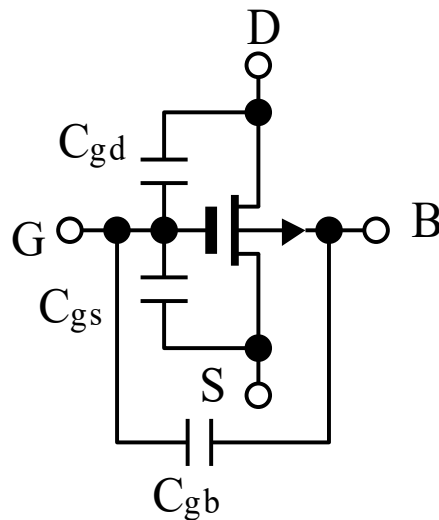
# Inter-electrode capacitance

The parasitic capacitances  $C_{gc}$ ,  $C_{gso}$ ,  $C_{gdo}$ ,  $C_d$  cause the equivalent inter-electrode capacitances  $C_{gs}(V)$ ,  $C_{gd}(V)$ ,  $C_{gb}(V)$ .



n-ch MOSFET

 


p-ch MOSFET

[Note] The inter-electrode capacitances are modeled in MOSFET device model of circuit simulator.

# Capacitance model in subthreshold region

When  $V_{gsn} < V_{tn0}$ ,

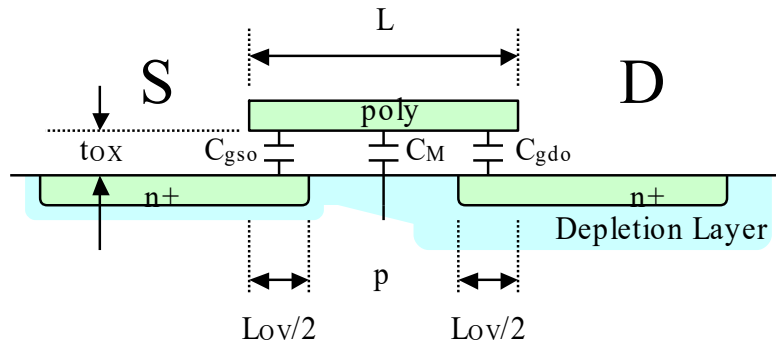

There is no channel.


$$C_{gs} = \frac{L_{OV}}{2} W \cdot C_{OX}$$

$$C_{gd} = \frac{L_{OV}}{2} W \cdot C_{OX}$$

} Overlap capacitance


$$C_{gb} = C_M = \frac{C_{OX} \cdot Cd}{C_{OX} + Cd}$$

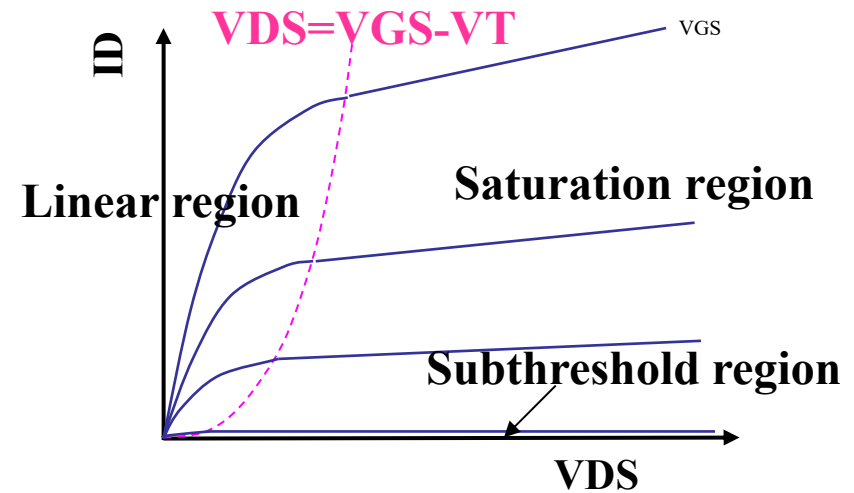Series connection of a gate oxide capacitance and a depletion layer capacitance



# Capacitance model in linear region

When  $V_{gsn} - V_{tn0} > V_{dsn}$ ,

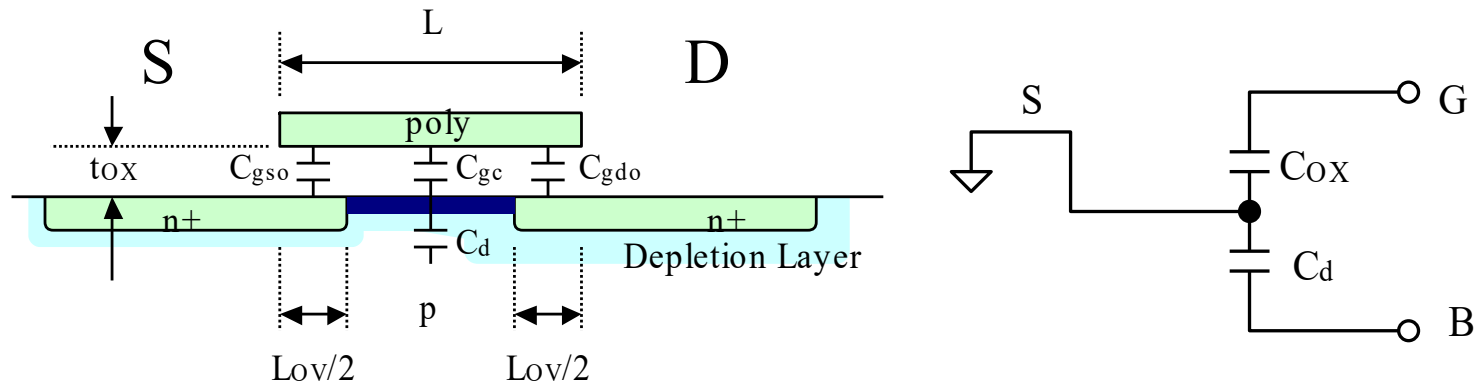

The channel is distributed in evenly.

$$C_{gs} = C_{gd} = C_{gso} + \frac{C_{gc}}{2} = \frac{L_{OV}}{2} W \cdot C_{OX} + \frac{1}{2} (L - L_{OV}) \cdot W \cdot C_{OX}$$


$$C_{gb} = \frac{C_{OX} \cdot Cd}{C_{OX} + Cd} \approx 0$$

Each one half of  $C_{gc}$  is assigned to the source electrode and the drain electrode.



# Capacitance model in saturation region

When  $V_{gsn} - V_{tn0} < V_{dsn}$ ,

 

- The  $3/2C_{gc}$  is assigned to the source electrode.
- The  $C_{gc}$  is not connected to the drain electrode due to the pinch-off effect.


The channel is distributed in evenly.

$$C_{gs} = C_{gso} + \frac{2}{3}C_{gc} = \frac{L_{OV}}{2}W \cdot C_{OX} + \frac{2}{3}(L - L_{OV}) \cdot W \cdot C_{OX}$$

$$C_{gd} = C_{gdo} = \frac{L_{OV}}{2}W \cdot C_{OX}$$

$$C_{gb} \approx 0$$

# Junction capacitance

 


Junction capacitance

$$C_j = \{b \cdot c + 2(b + c) \cdot x_j\} \cdot C_{j0}$$

Junction capacitance per unit area


$$C_{j0} = \sqrt{\frac{q \epsilon_0 \epsilon_{Si} N_A N_D}{2 \phi_B (N_A + N_D) (1 - V_{pn} / \phi_B)}}$$

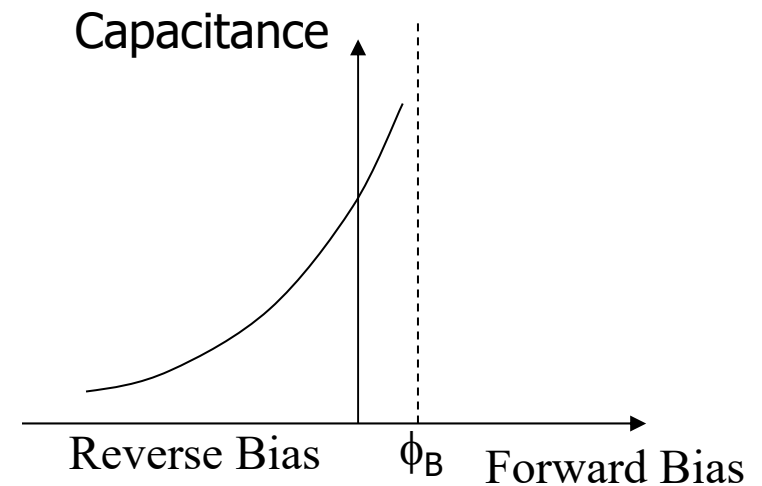$\phi_B$ : Built-in Potential  $\doteq 0.6V$



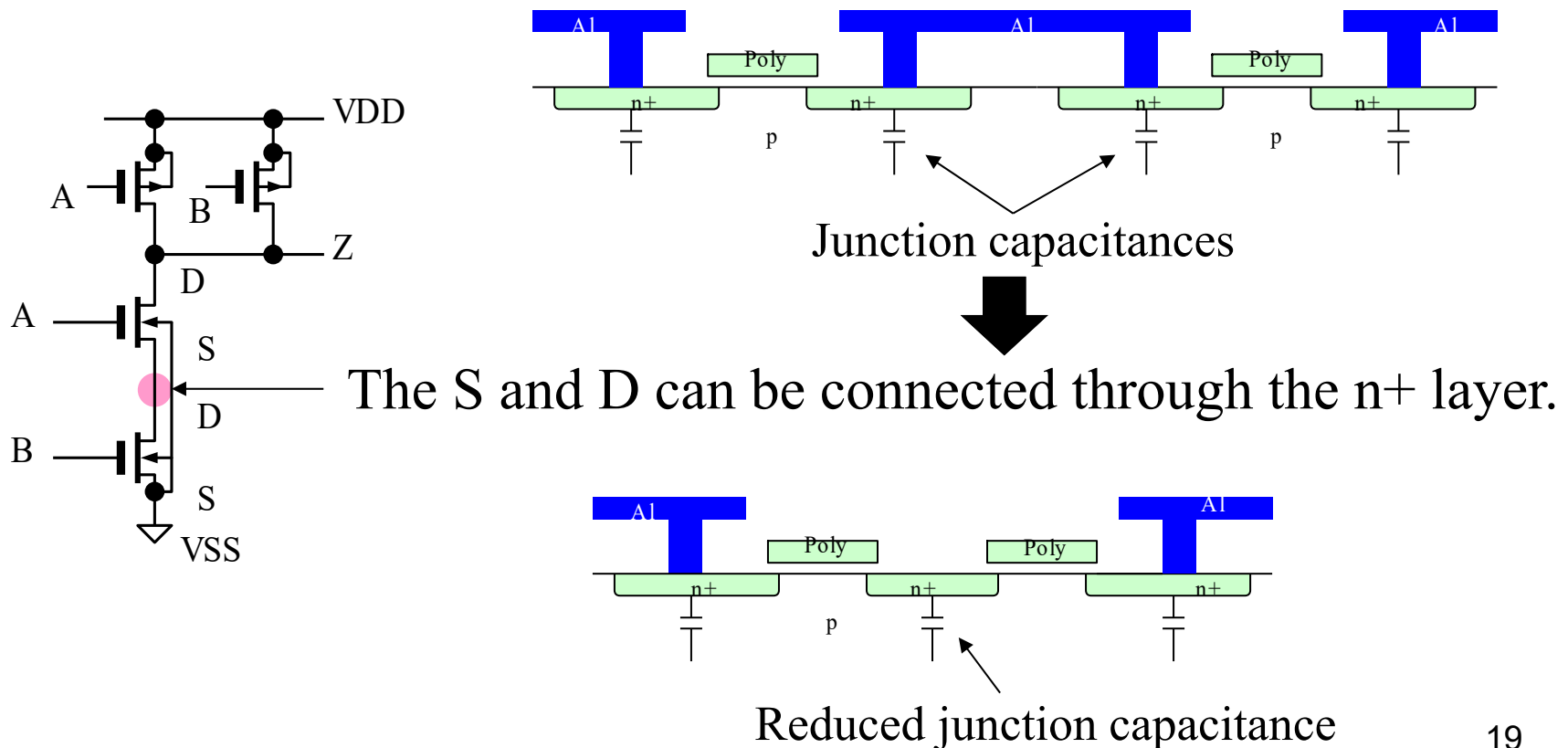
# Reduction of junction capacitance


The junction capacitance causes the load of MOSFET. The junction capacitance can be reduced by the direct connection of MOSFETs.




# Layout example of direct connection

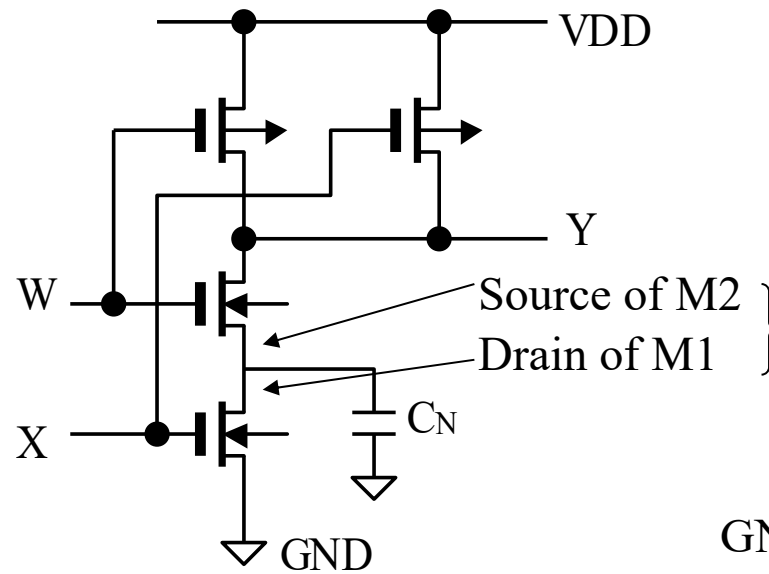

 The parasitic capacitance  $C_N$  is reduced by reducing the active area between the gates X and W.




# Parasitic capacitance in wiring layer

 

$$C_{in} = \epsilon_{FOX} \epsilon_0 \frac{w \cdot l}{t_{OX}} = w \cdot l \cdot C_{FOX}$$

$C_{FOX}$ : Parasitic capacitance per unit area

Numerical example

 


Parasitic resistance  $R_{in} = 100\text{m}\Omega \cdot \frac{100\mu\text{m}}{0.5\mu\text{m}} = 20\Omega$

Parasitic capacitance  $C_{in} = 200\text{fF}/\text{mm} \cdot 0.1\text{mm} = 20\text{fF}$

 
# Parasitic capacitance in multilayer wiring

- $C_{ww}$ : Metal-metal capacity
- $C_s$  : Metal-substrate capacity
- $C_s = C_{pp} + \sum C_f$
- $C_{pp}$  : Parallel plate capacity
- $C_f$  : Fringe capacity



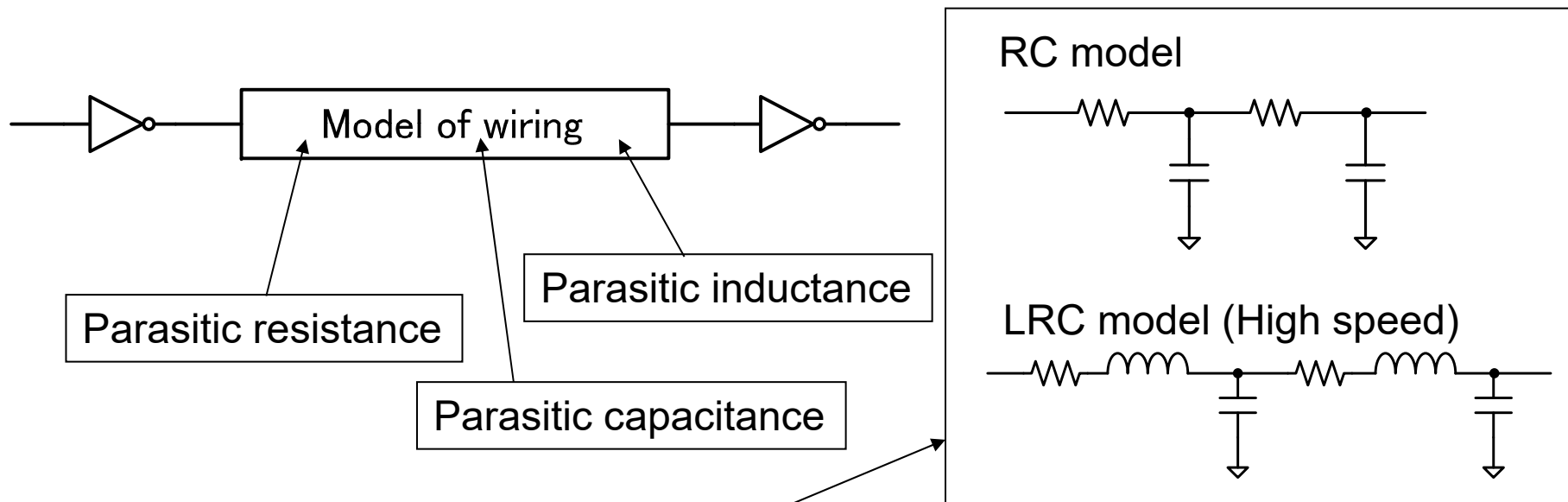
# Equivalent circuit of wiring

The equivalent circuit model of wiring is used for the detailed estimation of the delay time requires



The long wiring, such as BUS, clock line, Word line and Bit line in memory array, can be modeled by using the RC or LRC ladder network.

# Summary of parasitic devices

 


- Parasitic elements in MOSFET
  - is modeled in the MOSFET model. The parasitic capacitances and the parasitic resistances are reflected on the circuit simulation by using the size parameters of MOSFET.
- Parasitic elements in wiring
  - is distributed in the wiring field. The equivalent circuit model is manually or automatically generated by extracted by [LPE \(Layout Parasitic Extraction or Layout Parameter Extraction\)](#).



## 6.1.4 Transient response of CMOS logic


Delay time analysis of CMOS logic and driver circuit for speeding up

# Cause of rise time and fall time

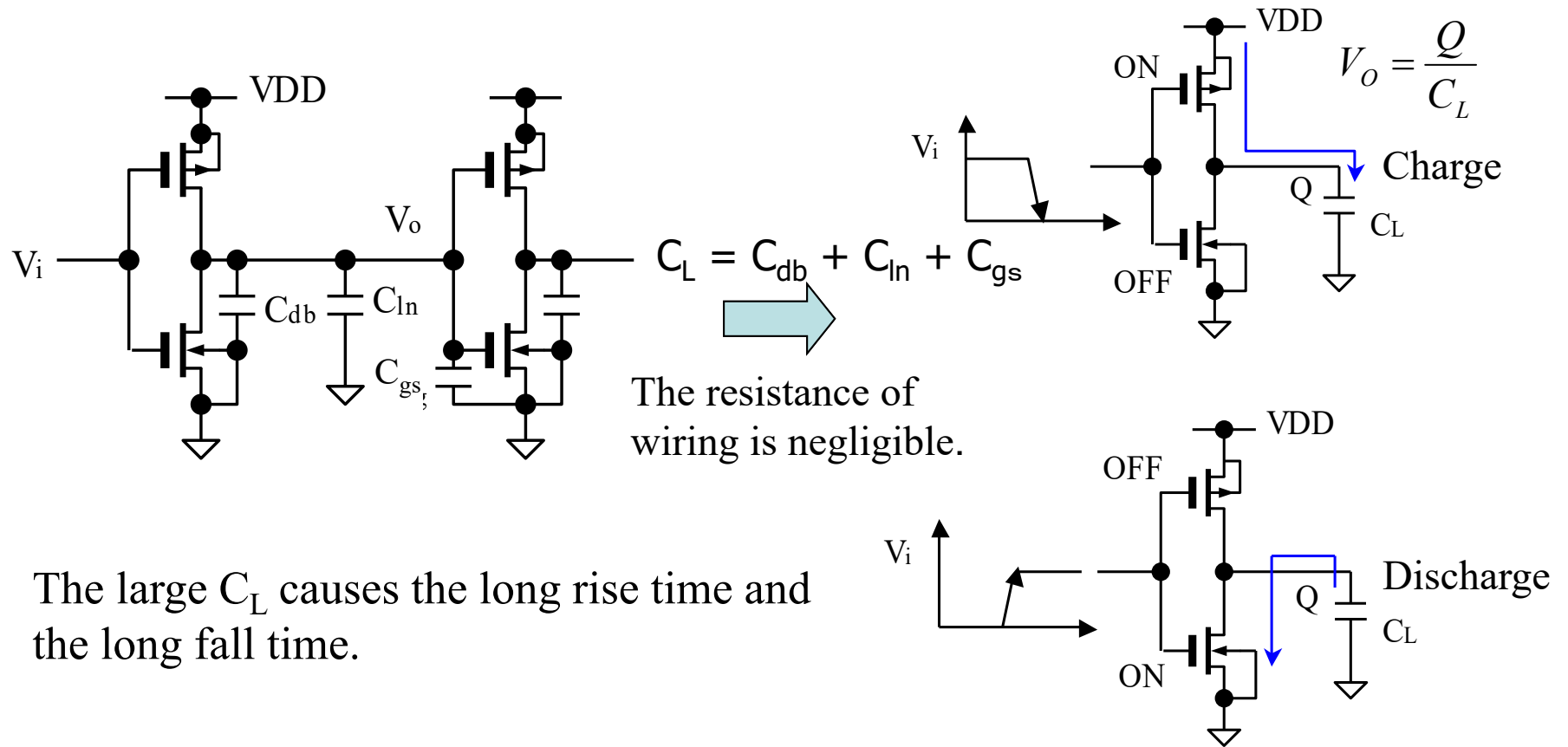


# Definition of rise time and fall time

Transient response of inverter

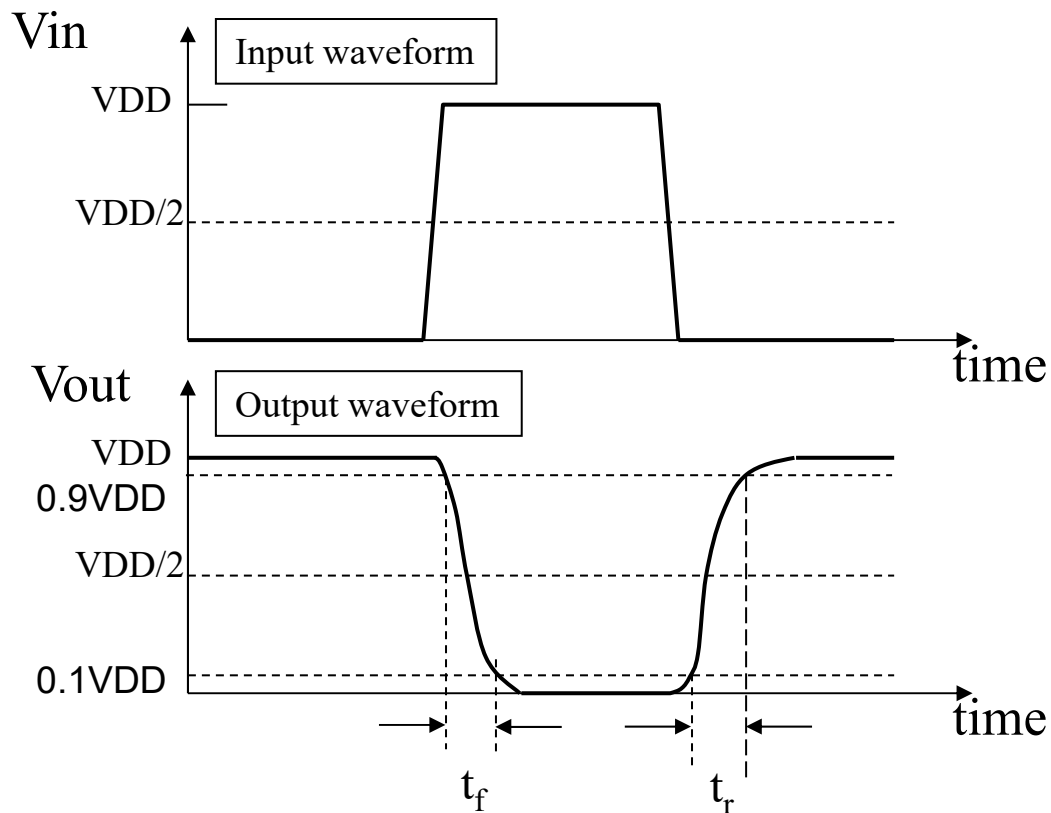

$t_f$  : Fall time  
 $t_r$  : Rise time

# Cause of propagation delay

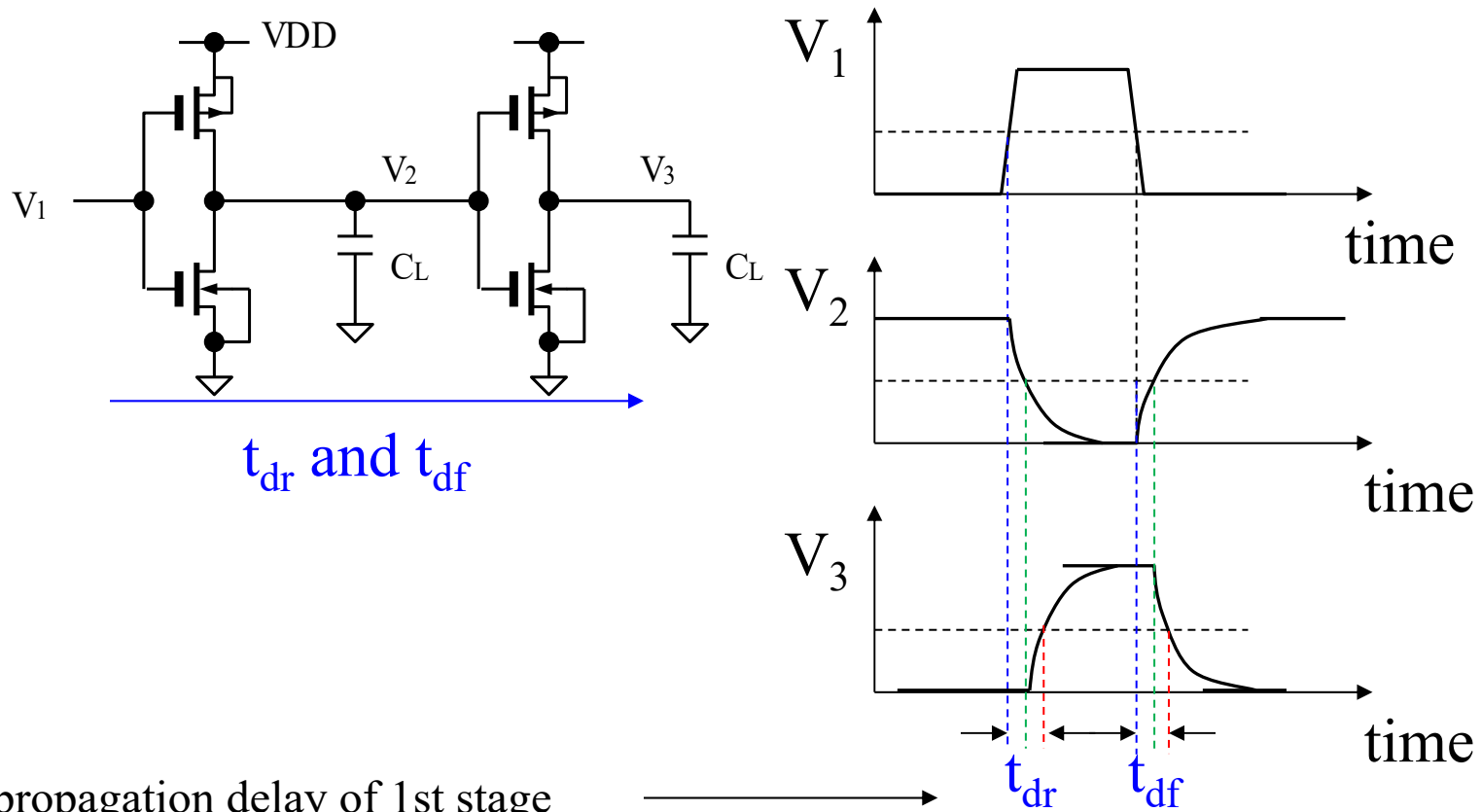


The propagation delay of 1st stage

A multi-stage logic circuit accumulates the delay time of gates. On the other hand, the rise time and fall time do not depend on the number of stages.


# Definition of propagation delay time

Transient response of inverter

 


Average delay time  $t_d = \frac{t_{df} + t_{dr}}{2}$

In the case of N-stage gate

 

Total delay time  $t_{total} = \sum_{n=1}^N t_{d_n}$


# Spikes

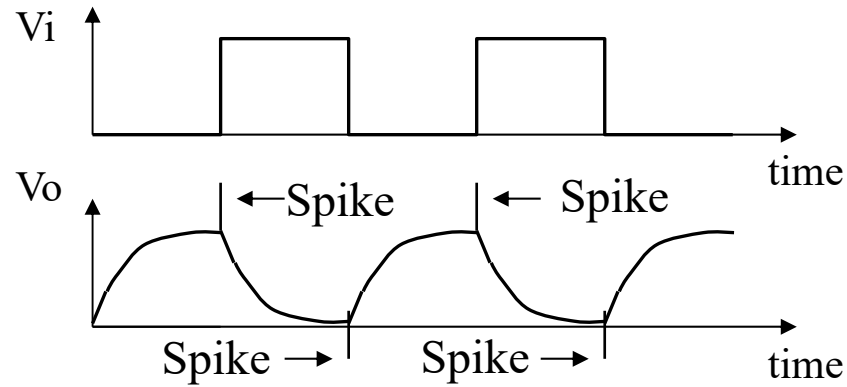

A parasitic capacitance in CMOS logic causes spikes. The spikes may be the cause of the malfunction of the circuits.

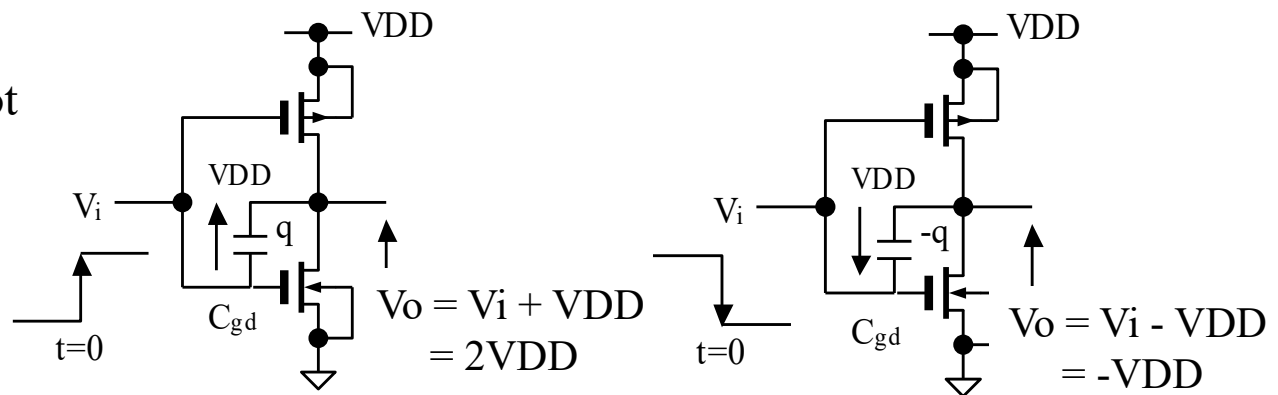
## Clock Feedthrough

The charge  $q$  on cannot instantly escape from  $C_{gd}$  and the output voltage  $V_o$  is doubled momentarily.



# Transient response of MOSFETs

States of MOSFETs X1 - X2 - X3 - X4 - X5

 

State	X1	X2,X3	X4,X5	X6
n-ch	Subthreshold	Saturation	Linear	Linear
p-ch	Linear	Subthreshold	Subthreshold	Subthreshold

# Current in MOSFET in the transient response


States	Current of n-ch MOSFET	Output voltage
X1→X2 (Subthreshold to Saturation)	Momentary transition (Direct path short current, See the latter chapter)	VDD (Constant)
X2→X3→X4 (Saturation)	$\frac{\beta_n}{2}(VDD - V_{th0})^2$	$-\frac{\beta_n}{2C_L}(VDD - V_{th0})^2 t + VDD$
X4→X5→X6 (Linear)	$\beta_n \left\{ (VDD - V_{th0}) \cdot V_o - \frac{1}{2} V_o^2 \right\}$	$\frac{2(VDD - V_{th0})}{\exp\left\{\frac{\beta_n}{C_L}(VDD - V_{th0})t\right\} + 1}$

[Note] cf. Appendix 4 for the detailed calculation.


 
# Calculation of rise and fall time

Output wave form (but practically, there is no angle at X4.)



$$\left\{ \begin{array}{l} t_f = t_{f1} + t_{f2} = \frac{2C_L}{\beta_n(V_{DD} - V_{tn0})} \left\{ \frac{V_{tn0} - 0.1 \cdot V_{DD}}{V_{DD} - V_{tn0}} + \frac{1}{2} \ln \left( \frac{1.9 \cdot V_{DD} - 2 \cdot V_{tn0}}{0.1 \cdot V_{DD}} \right) \right\} \\ t_r = t_{r1} + t_{r2} = \frac{2C_L}{\beta_p(V_{DD} + V_{tp0})} \left\{ \frac{-V_{tp0} - 0.1 \cdot V_{DD}}{V_{DD} + V_{tp0}} + \frac{1}{2} \ln \left( \frac{1.9 \cdot V_{DD} + 2 \cdot V_{tp0}}{0.1 \cdot V_{DD}} \right) \right\} \end{array} \right.$$

# Methods for reducing the rise time and fall time

$C_L$	Small
$\beta_{n/p}$ or $W_{n/p}/L_{n/p}$	Large
VDD	Large

[Note] The load capacitance  $C_L$  depends in the W/L of MOSFET. The large  $\beta_{n/p}$  and the small  $C_L$  is incompatible. According to the further analysis,

$$\frac{\left(\frac{W_n}{L_n}\right)}{\left(\frac{W_p}{L_p}\right)} = \sqrt{\frac{\mu_p}{\mu_n}} \quad \text{for minimum time of } t_r + t_f$$

FYI, for maximum noise margin

$$\begin{cases} V_{tn0} = |V_{tp0}| \\ \beta_n = \beta_p \end{cases} \quad \beta_n = \mu_n C_O \frac{W_n}{L_n}, \beta_p = \mu_p C_O \frac{W_p}{L_p} \rightarrow \frac{\left(\frac{W_n}{L_n}\right)}{\left(\frac{W_p}{L_p}\right)} = \frac{\mu_p}{\mu_n}$$

# Maximum operating frequency of gate

Definition of the maximum operating frequency  $f_{max}$

$$f_{max} \approx \frac{1}{T_{min}} = \frac{1}{t_r + t_f} \text{ (Hz)}$$

When the pulse width is lower than  $t_r + t_f$ , the logic swing is decreased from  $V_{OH} - V_{OL}$ .


## Example

When  $V_{tn0} = 0.2VDD$  and  $V_{tp0} = -0.2VDD$ ,


$$t_f = \frac{3.70C_L}{\beta_n VDD}$$

$$t_r = \frac{3.70C_L}{\beta_p VDD}$$
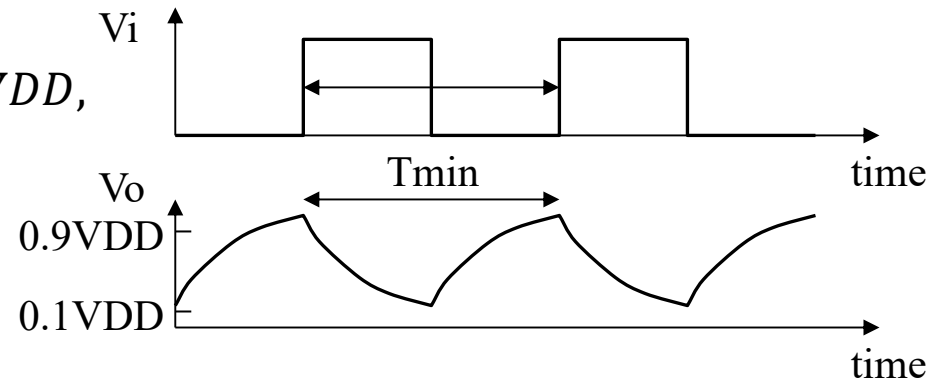
$$f_{max} = \frac{VDD}{3.70C_L} \frac{\beta_n \beta_p}{\beta_n + \beta_p}$$




# Fan-out 1

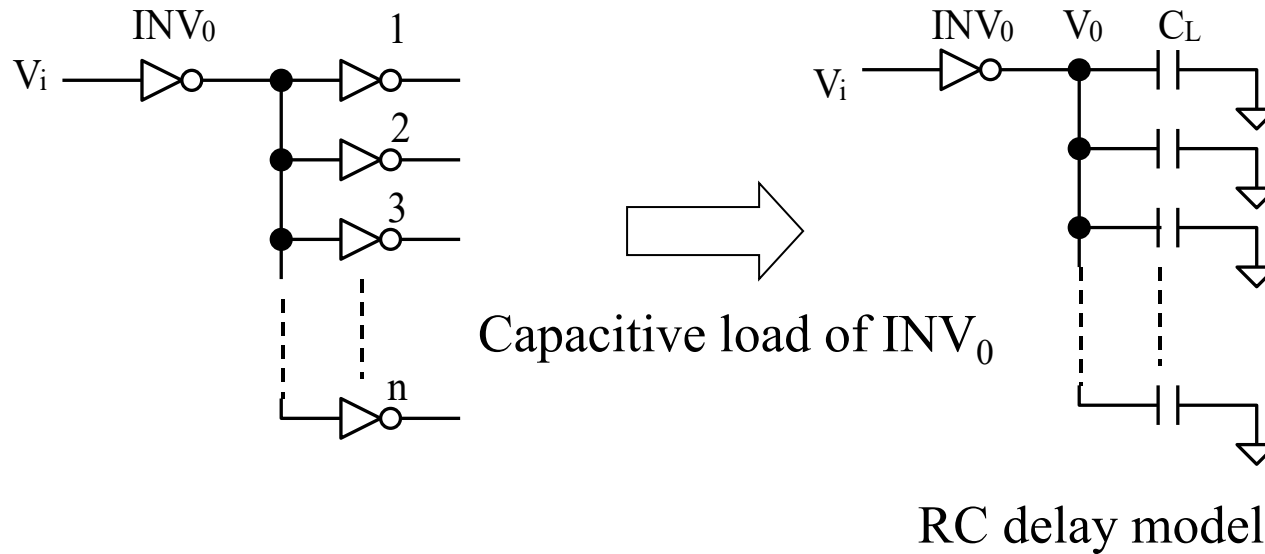


Number of fan-out  
 $n_{fo} = \text{Number of gate in the next stage}$

 The total load of  $INV_0 = n_{fo} C_L$ .  
 The large  $n_{fo}$  causes the long charging time.


 
# Fan-out 2

A delay time is proportional to on the number of stages and fan-out. However, it should be noted that the number of stages and fan-out is incompatible. **The small number of stages is not always optimum for the high-speed operation.**




The intrinsic delay time  $t_0$  (**Parasitic delay**) is observed even if  $n_{fo} = 0$ . The parasitic capacitance on the output node of the gate causes  $t_0$ .

[Note] The parasitic capacitance of wiring is added to the total load of the gate. This disturbs the proportional relationship between  $t_d$  and  $n_{fo}$ .
 
# Multistage driver

A large capacitive load, e.g. data bus, cannot drive at a high speed by the small inverter (with small W/L of MOSFET). A buffer consisted cascaded inverters is applied to decrease the delay time.

The size ratio  $W_{N+1}/W_N$  of MOSFET per 1-stage is  $u$ .



For input capacitance of gate  $C1$ ,  
Load  $CL$ , effort  $x$ ,

$$CL = x \cdot C1$$

The input capacitance and the output current  
are proportional to the size of MOSFET.

$$\begin{cases} C_n = u^n C1 \\ I_n = u^{n-1} I1 \end{cases}$$

$$\text{Delay time of } n^{\text{th}}\text{-stage } t_{dn} = \frac{C_n}{I_n} = \frac{u^n C1}{u^{n-1} I1} = u \cdot t_{d1} \quad 38$$

# Optimization of MOSFET size

When the load capacitance  $C_L$  can be drive by N-stage driver.


$$CL = u^N \cdot C1 = x \cdot C1 \quad \Rightarrow \quad N = \frac{\ln x}{\ln u}$$

$$\text{Total delay time: } t_d = \sum_{n=1}^{N-1} t_{dn} = N \cdot u \cdot t_{d1} = u \frac{\ln x}{\ln u} t_{d1}$$

The total delay time is minimized by the optimization of  $u$ .


$$\frac{\partial t_d}{\partial u} = \frac{\ln x}{\ln u} t_{d1} \left( 1 - \frac{1}{\ln u} \right) = 0$$

$$\therefore u = e = 2.7182 \dots$$

 


The output capacitance is ignored in this calculation. The drain capacitance of (n-1)<sup>th</sup> stage should be added to the input capacitance of n<sup>th</sup> stage as a load capacitance of the (n-1)<sup>th</sup> stage. When the input capacitance and output capacitance is considered, [the optimum value of u is 3.59](#).

# Input buffer

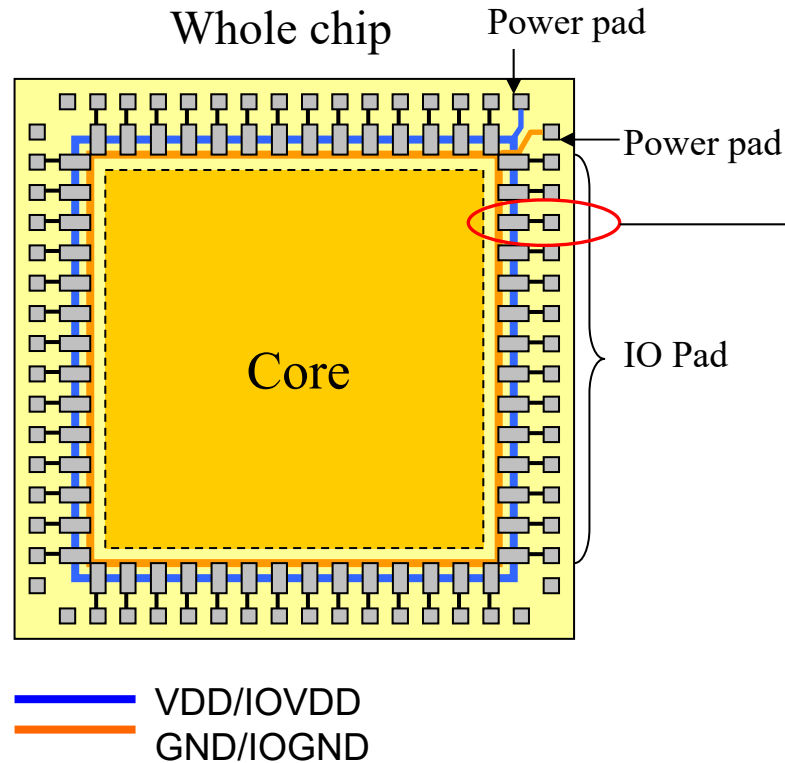

IO buffer + Power ring + Pad

 - Input buffer = ESD protection
- Output buffer = Multistage driver





ESD (Electrostatic Discharge)

[Note] Normally, the power pads and the power lines for IO circuit are independently provide from the power line of core circuit.



# Output buffer

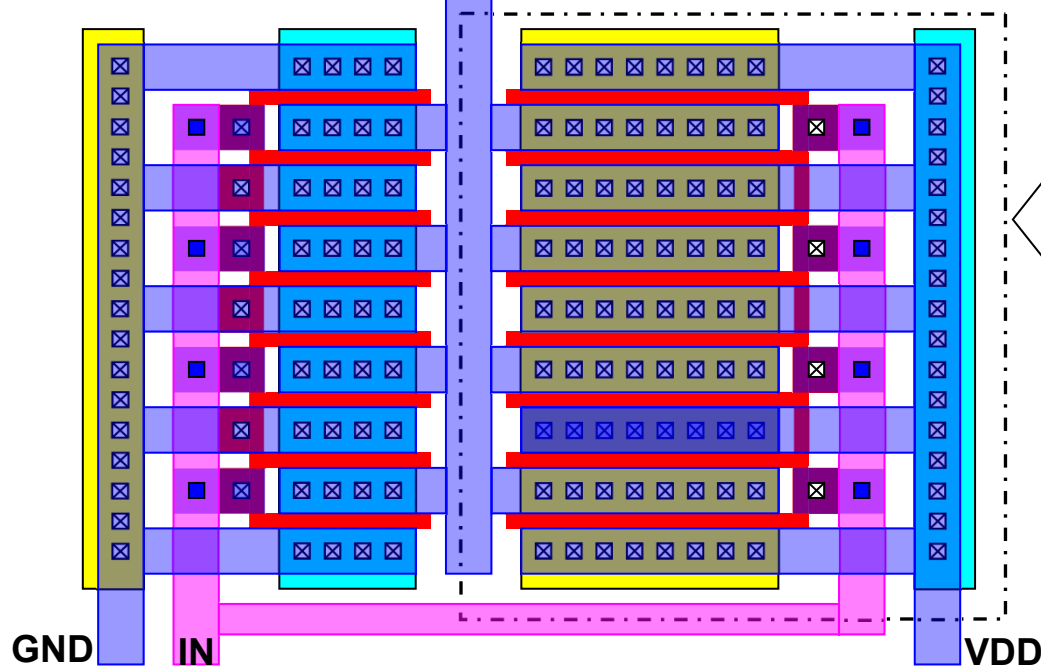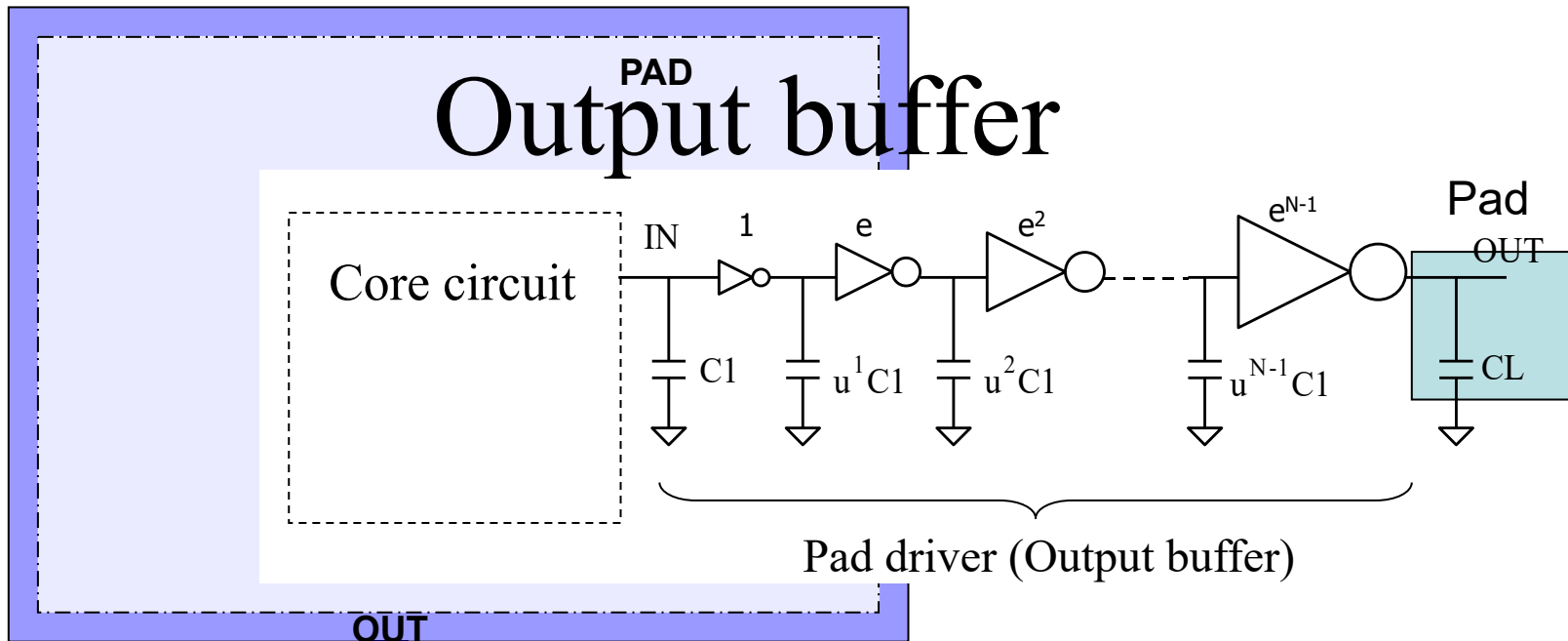

Layout example of output buffer

If you want to implement a bidirectional buffer, replace a last stage of a cascaded inverter with a tristate buffer.